


amateur radio

Vol. 37, No. 12

DECEMBER, 1969

Registered at G.P.O. Melbourne, for
transmission by post as a periodical

PRICE 30 CENTS

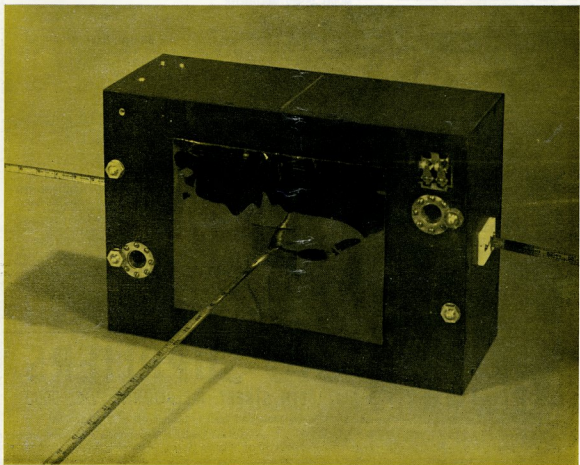

Merry Christmas and Happy New Year to all our Clients

REALISTIC DX-150 SOLID STATE COMMUNICATIONS RECEIVER

Features: 240v a.c. or 12v d.c. operation, 30 transistors and diodes. 535 Kc. to 30 Mc. in four bands. Bandspread tuning. "S" meter, a.m./c.w./s.b. Product detector for s.b. Compact size, 14½ x 9¼ x 5½ in. Polished metal panel, small internal speaker.

F.O.R. Price \$229.50

Matching external speaker £13.30 extra.

No. 62 TRANSCEIVERS

Wireless Set No. 62 Mk. 2 (Pye). Frequency range 1.5 to 10 Mc. in two bands, in-built 12v. generator power supply. Clean condition. Fully air tested on transmit and receive.

F.O.R. Price \$49.50 inc. circuit diagram

WESTON LM-300 MOBILE TAXI RADIO

Low Band a.m. 60 Kc. bandwidth, 70-80 Mc. Crystal channel locked, single channel. In-built transistor power supply, 12v. operation, suit country taxi service or conversion to Ham bands, inc. microphone and cradle.

F.O.R. Price \$45. Packing 50c

AS NEW AND AIR TESTED

LAFAYETTE 5W. C.B. TWO-WAY RADIO*

Model HE-20, fully transistorised, solid state, 13 transistors, 10 diodes, 27.240 Mc. Provision for 23 channels, crystal channel locked, push-pull audio modulator, 455 Kc. mechanical filter, spotting switch for accurate reception, t.v. trap, 230v. a.c. and 12v. (positive or negative ground), in-built p.a. amplifier. Ideal for fixed base station or emergency mobile, including microphone and mobile cradle. Fibreglass helmet aerial 4 ft. high, cow mount. *Subject to P.M.G. approved licence.

F.O.R. Price \$169.50 tax paid for mobile use \$816.50 extra.

BENDIX BC-221 FREQ. METER

125 Kc. to 20 Mc., including a.c. power supply, crystals, calibration book, etc.

F.O.R. Price \$49.50, packing 75c

TRIO COMM. RECEIVER MODEL 9R-59DE

Four-band receiver covering 550 Kc. to 30 Mc. Continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valves plus 7 diode circuit, 4/8 ohm output and phone jack. SSB-CW, ANL, variable BFO, S meter, sep. bandspread dial, i.f. 455 kc., audio output 1.5w., variable RF and AF gain controls, 115/250v. AC mains. Beautifully designed. Size: 7 x 15 x 10 in. With instruction manual and service data.

PRICE \$175 inc. sales tax

Speaker to suit, type SP5D, \$15 inc. tax.

MULTIMETERS

MODEL C-1000 POCKET MULTIMETER

1000 ohms per volt. AC volts: 0-10, 50, 250, 1000. DC volts: 0-10, 50, 250, 1000. DC current: 0-100 mA. Resistance: 0-15K ohms (5K centre). Two colour scale. Range selector switch. Dimensions: 3½ x 2¼ x 1 in.

Price \$6.50 post free

MODEL 200H MULTIMETER

20,000 ohms per volt. DC volts: 0-5, 25, 50, 250, 500, 2500 (20,000 o.p.v.). AC volts: 0-15, 50, 100, 500, 1000 (10,000 o.p.v.). DC current: 50 µA, 2.5 mA, 250 mA. Resistance: 0-60K/6M ohm (scale centre 300, 30K ohm). Capacitance: 10 pF to 0.061 µF/0.001 µF to 0.1 µF. Db. scale: -20 db. to plus 22 db. Size 4½ x 3½ x 1½ in.

Price \$11.25 post 30c

MODEL CT330 MULTIMETER

20,000 ohms per volt. DC volts: 0-6, 30, 120, 600, 1.2K, 3K, 6K. AC volts: 0-6, 30, 120, 600, 1.2K (10K o.p.v.). DC current: 0-0.05 mA, 60 mA, 600 mA. Resistance: 0-6K, 60K, 6M, 60M/60M ohm (30, 3K, 30K, 300K centre scale). Capacitance: 30 pF to 0.001 µF, 0.001 µF to 0.2 µF. Decibels: -20 to plus 63 db. Size approx. 5½ x 3¼ x 1½ in.

Price \$16.75 post 30c

MODEL OL-64D MULTIMETER

20,000 ohms per volt. DC volts: 0.025, 1, 10, 50, 250, 500, 1000 (at 20K o.p.v.). 5000 (at 10K o.p.v.). AC volts: 0-10, 50, 250, 1000 (at 8K o.p.v.). DC current: 50 µA, 1 mA, 10 mA, 500 mA, 10 amps. Resistance: 0-4K, 40K, 4M, 40 Megohm. Db. scale: -20 to plus 36 db. Capacitance: 250 pF to 0.02 µF. Inductance: 0-500 H. Size 5¼ x 4¼ x 1¼ in.

Price \$19.50 post 30c

NEW MODEL US-100

Overload protection. Shockproof movement. Polarity switch. DC volts: 0-0.25, 1, 25, 10, 50, 250, 1000 (20K o.p.v.). AC volts: 0-2.5, 10, 50, 250, 1000 (5K o.p.v.). DC current: 1 mA, 25 mA, 500 mA, and 10 amp. AC current: 10 amp. Resistance: 0-50M ohm (centre scale 50). 1, 10, 100, 1K, 10K, 50 K. Db. scale: -20 to plus 10, plus 22, plus 25, plus 50 db.

Price \$28.75 post 40c

MIRROR SCALE

MODEL AS100/DP HIGH SENSITIVITY

100,000 ohms per volt DC. Mirror scale, protected movement. DC volts: 3, 12, 60, 120, 300, 600, 1200 (100K o.p.v.). AC volts: 8, 40, 120, 300, 600, 1200 (10K o.p.v.). DC current: 12 µA, 5 mA, 60 mA, 300 mA, 12 amps. Resistance: 2K, 20K, 20M, 200Megohm. Decibels: -20 to plus 63 db. Audio output: 6, 30, 120, 300, 600, 1200 volts a.c. Size 7½ x 5½ x 2¼ in.

Price \$34.50 post 75c

MODEL A10/P GIANT (6½ inch) METER, CIRCUIT TESTER

30,230 ohms per volt DC with in-built signal injector, overload protected. DC volts: 0.5, 2.5, 10, 50, 250, 500, 1000 (at 30K o.p.v.). 5000 (at 10K o.p.v.). AC volts: 2.5, 10, 50, 250, 500, 1000 (at 10K o.p.v.). DC current: 50 µA, 5 mA, 50 mA, 500 mA, 1 amp., 10 amp. AC current: 1 amp., 10 amp. Resistance: 10K, 100K, 1M, 10 Megohm. Signal Injector: Blocking oscillator circuit with a 22A102 Trans. Decibels: -20 to plus 53 db. Size: 6½ x 7¼ x 3¼ in.

Price \$55 tax paid, post 75c

TE-16A TRANSISTORISED TEST OSCILLATOR

Frequency range: 400 Kc. to 30 Mc. in five bands. Modulated 800 c/s. sine wave. Modulation: 30 p.p.m. approx. Output Imp.: Low impedance. Dimensions: 5½ x 5½ x 3¼ in. Weight: 1.5 lb.

Price \$24 tax paid, post 75c

"NIKKA" 1 WATT TRANSCEIVERS

P.M.G. approved. Solid state, 14 transistors, circuit inc. r.f. stage, 27.240 Mc. (provision for two channels). Range boost circuit. Up to 10 miles in open country or water. Buzzer type call system. Squelch control. Complete with leather carrying case.

Price \$175.00 Pair

NEW A.W.A. T.V. TUNER

Model 4983. Uses 6U8 and 6B07A.

Price \$5.50 postage 50c

PACK OF RESISTORS

100 Resistors of ½ and 1 watt rating.

Price \$1.75 post 20c

BRAND NEW SPEAKERS

		Price	\$1.75	Postage	20c
2½ inch	8 ohms	..	\$2.00	..	20c
3 inch	8 ohms	..	\$2.25	..	20c
4 inch	8 ohms	..	\$2.25	..	20c
4 inch	15 ohms	..	\$2.25	..	20c
3DX	8 ohms	..	\$3.95	..	20c
3DX	15 ohms	..	\$3.95	..	20c
6AT	8 ohms	..	\$5.50	..	40c
6AT	15 ohms	..	\$5.50	..	40c
8A7	8 ohms	..	\$7.20	..	40c
8A7	15 ohms	..	\$7.20	..	40c
12A9	8 ohms	..	\$18.75	..	50c
12A9	15 ohms	..	\$18.75	..	50c

Nett Price

NEW STEREO HEADPHONES

Large rubber earpiece. Frequency range 100 to 1500 cycles, 8 ohms impedance.

Price \$6.75 post 30c

DELCO TRANSISTORS

Type 2N441	...	Price \$2.40	postage 10c
Type 2N278	...	Price \$6.00	postage 10c
Type 2N301	...	Price \$2.50	postage 10c

LT91 RECTIFIER

20 Volt 2 Amp.

Price \$1.50 post 10c

RADIO SUPPLIERS

323 ELIZABETH STREET, MELBOURNE, VIC., 3000

Phones: 67-7329, 67-4286 All Mail to be addressed to above address

We sell and recommend Leader Test Equipment, Pioneer Stereo Equipment and Speakers, Hitachi Radio Valves and Transistor Radios, Kew Brand Meters, A. & R. Transformers and Transistor Power Supplies, Ducon Condensers, Welwyn Resistors, etc.

amateur radio

JOURNAL OF THE WIRELESS INSTITUTE OF AUSTRALIA FOUNDED 1910



DECEMBER 1969

Vol. 37, No. 12

Publishers:

VICTORIAN DIVISION W.I.A.
Reg. Office: 478 Victoria Parade, East Melbourne, Vic., 3002.

Editor:

K. E. PINGOTT VK3AFJ

Assistant Editor:

E. C. Manifold VK3EM

Publications Committee:

A. W. Chandler VK3LC
Ken Gillespie VK3GK
Peter Ramsay VK3ZWN
W. E. J. Roper (Secretary) VK3ARZ

Circulation—

Jack Kelly VK3AFD

Draughtsmen—

Clem Allan VK3ZIV
John Blanch VK3ZOL
John Whitehead VK3YAC

Enquiries:

Mrs. BELLAIRS, Phone 41-3535, 478 Victoria Parade, East Melbourne, Vic., 3002. Hours: 10 a.m. to 3 p.m. only.

Advertising Representatives:

AUSTRALIAN MEDIASERV
21 Smith St., Fitzroy, Vic., 3065. Tel. 41-4662.
P.O. Box 108, Fitzroy, Vic., 3065.

Advertisement material should be sent direct to the printers by the first of each month.

Advertisements should be addressed to the Editor.

Printers:

"RICHMOND CHRONICLE," Phone 42-2419.
Shakespeare Street, Richmond, Vic., 3121.



All matters pertaining to "A.R." other than advertising and subscriptions, should be addressed to:

THE EDITOR,
"AMATEUR RADIO,"
P.O. BOX 38,
EAST MELBOURNE, VIC., 3002.



Members of the W.I.A. should refer all enquiries regarding delivery of "A.R." direct to their Divisional Secretary and not to "A.R." direct. Two months' notice is required before a change of mailing address can be effected. Readers should note that any change in the address of their transmitting station must, by P.M.S. regulation, be notified to the P.M.S. in the State of residence; in addition, "A.R." should also be notified. A convenient form is provided in the "Call Book".

CONTENTS

Technical Articles:—

	Page
Conversion of Circuit Diagrams to Veroboard, Tag-Board and Printed Circuit Layout	12
High Voltage Regulators	15
More on the Single Loop, Triband Cubical Quad Beam Element	20
Sideband the Expensive Way (how to avoid it)	10
The F.M. System	7
The W8NWU Teeter Totter Tuners	17
Transistors on Computer Boards—Some Further Thoughts	21

General:—

Australis Oscar 5 Progress Report	18
Book Review	27
Burglary at VK2WI (Dural) and also at Crows Nest	24
Comment	6
Correspondence	26
DX	30
Federal Awards	32
Index to Volume 37—1969	36
Intruder Watch Notes	32
Joe	14
New Equipment	26
Observations from Australis Oscar 5	19
Overseas Magazine Review	28
Prediction Charts for December 1969	27
VHF	31
W.I.A. DX.C.C.	16
W.I.A. V.H.F.C.C.	32

Contests:—

Contest Calendar	32
John Moyle Memorial National Field Day Contest, 1970	25

COVER STORY

The Australis Oscar 5 Satellite. The yellow section in centre is a thermal blanket designed to maintain internal temperature at 70°F. Black paint protects the chromium plating which covers remainder of the satellite and will be removed shortly before launching.

approved
&
accepted

by leading manufacturers and
Government Departments

ELNA

ELECTRONIC COMPONENTS

- Electrolytic Capacitors
- Polyester Capacitors
- Carbon Potentiometers

Australia's largest selling im-
ported capacitors are produc-
ed by one of the world's major
components manufacturers



Write or phone for
illustrated brochure

SOANAR
ELECTRONICS
PTY. LTD.

A & R-Soanar Group of Companies

VIC: 45 Lexton Rd., Box Hill; 89-7323.
NSW: 82 Carlton Cr., Summer Hill; 798-0999.
QLD: R. A. Venn Pty. Ltd., Valley; 51-5421.
SA: Scott Thompson Pty. Ltd., Adelaide;
23-2261.
WA: Everett Agency Pty. Ltd., West Leade-
ville; 8-4137.




EDDYSTONE

Model "EA12"

Amateur Band Communications Receiver

The EDDYSTONE "EA12" is a model specially designed for use by Amateur Radio operators and covering the six major Amateur bands from 1.8 to 28 Mc. It possesses an exceedingly good electrical performance and will produce first-class results with all modes of signals. Mechanically the "EA12" is built to the high engineering standards common to all Eddystone products and will give years of trouble-free service, irrespective of climate.

Write for Technical Leaflets

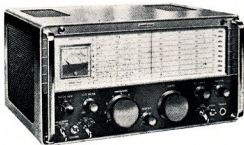

FEATURES—

- Adequate bandsread, correct degree of selectivity for the various modes of signal, ease of tuning S.S.B. signals, and frequency stability.
- Cascode type R.F. amplifier stage.
- Separate R.F., I.F. and A.F. gain controls.
- Continuously variable selectivity in the 100 Kc. second I.F. stages. Crystal filter can be switched in to give an extremely narrow band for c.w.
- Mode switch selects either upper or lower sideband.
- Large S meter, calibrated from 1 to 9, each division 6 db. change of level.
- Two noise limiters, one a series diode type for a.m., other a double diode which is operative with c.w. and s.s.b.
- Image rejection better than 50 db. at highest frequency and proportionally greater at lower frequencies.

Sole

Agents:

R.H. Cunningham
PTY. LTD.

608 COLLINS ST., MELBOURNE, VIC., 3000.

Phone 61-2464

64 ALFRED ST., MILSONS POINT, N.S.W., 2061.

Phone 929-8066

34 WOLYA WAY, BALGA, PERTH, W.A., 6061.

Phone 49-4919

L. E. Boughen & Co., 30 Grimes St., Auchenflower, 4066. Ph. 7-4097



2N3055
FOR
IMMEDIATE
DELIVERY

FAIRCHILD
AUSTRALIA PTY. LTD.

SIDE BAND ELECTRONICS ENGINEERING

With the approach of the holidays period, usually the interest in mobile operation increases. I am ready for it, with stocks of YAESU MUSEN FT-DX-100 and FT-200, SWAN 350C and 500C Transceivers, plus DC Power Supplies for Swans and Galaxies and also for the FT-200! Also Webster Bandspanners and MARK Helical Whips will be in stock again.

Another interesting addition to my stock is the OMEGA Antenna Noise Bridge. This remarkable little unit takes the guess-work out of antenna tuning and feedline matching work—a must for the serious Amateur.

Substantial purchases during the December 1969 Christmas month will include a free bonus Christmas gift. A MERRY CHRISTMAS to all!

—Arie Bles

YAESU-MUSEN—

FT-DX-400 De Luxe Transceiver	\$525
FT-DX-100 AC/DC Transceiver	\$515
FV-400 Second External VFO	\$80
FT-200 Transceiver with 230/240/250v. AC heavy duty power supply-speaker unit in matching cabinet	\$410
FR-DX-400-SDX De Luxe Receiver with all the available extras and accessories—CW and FM filters, FM discriminator, 2 and 6 metre converters installed	\$475
FL-DX-400 Transmitter	\$375
FL-DX-2000 Linear Amplifier	\$225

SWAN—

SW-350C Transceiver, with SWAN AC/DC power supply, special package offer, if still in stock	\$600
SW-500-C Transceiver	\$675
AC Power Supply-Speaker Unit	\$80

GALAXY—

GT-550 Transceiver	\$650
External Second VFO	\$110
VOX Unit	\$35
Galaxy equipment on indent order only.	

HY-GAIN—

TH6DXX 6-element tri-band Yagi	\$180
BN-86 Balun	\$20
HY-QUAD tri-band Cubical Quad	\$140
TH3JR Junior 3-element tri-band Yagi	\$110
14AVQ 10 to 40 metre four-band Vertical	\$45
18AVQ 10 to 80 metre five-band Vertical	\$75

Crystal Filters, Co-ax. Cables and Connectors, SWR Meters, Tubes available as advertised last month.

All Prices are net Springwood, N.S.W., Sales Tax included, subject to change without prior notice.

USED EQUIPMENT

GALAXY V. with AC supply-speaker unit, VOX, Cal., excellent condition	\$375
HALLICRAFTERS PS-150-12 DC supply	\$75
HEATH HP-14 DC supply	\$75

J-BEAM LTD.—

TRIPLE-THREE full size 3-element tri-band Yagi with built-in 52 ohm balun, delivery delayed by the factory till January '70	\$180
---	-------

MOSLEY—

TA33JR Junior 3-element tri-band Yagi	\$95
MP-33 3-element tri-band Tiger Array	\$120

ROTATOR—

CDR HAM-M heavy duty Rotator, with 230v AC indicator-control unit	\$165
---	-------

A.C.I.—

ACITRON extra heavy duty 12V. DC supply for Galaxies, Swans, etc.	\$125
ACITRON heavy duty 12V. DC supply, especially made for the FT-200 ..	\$110

MOBILE WHIPS—

WEBSTER Bandspanners, 10 to 80 Metres	\$55
MARK HW-40 40 Metre Helical Whip	\$20
MARK HW-3 10/15/20 Metre instant tri-band Helical Whip	\$35
Whip swivel mount and spring	\$10

ANTENNA NOISE BRIDGE—

OMEGA TE 7-01 Noise Bridge	\$25
----------------------------------	------

CRYSTALS—

FT-241 series, channels 0 to 79, box of 80 xtls	\$17.50
Sets of four matched filter crystals, plus two matched USB/LSB carrier-BFO crystals—	
from 400 to 450 Kc.	\$5 to \$10
from 460 to 500 Kc.	\$10 to \$5

Sideband Electronics Engineering

P.O. BOX 23, SPRINGWOOD, N.S.W., 2777

Telephone (STD 047) 511-394 Springwood

professional or amateur... chart your course to varian/eimac for dependable, high quality power tubes

EIMAC TUBE TYPE	CLASS OF OPERATION SERVICE	TYPICAL OPERATION — SINGLE TUBE								FLUORENT VOLTS AMPERES
		D.C. PLATE VOLTAGE	D.C. PLATE CURRENT (AMPERES)	D.C. SCREEN VOLTAGE	D.C. GRID VOLTAGE	APPROX. MAX. DRIVE POWER (WATTS)	APPROX. D.C. SCREEN CURRENT (AMPERES)	APPROX. D.C. GRID CURRENT (AMPERES)	APPROX. MAX. POWER OUTPUT (WATTS)	
3-400Z	B SSB	3000	.100 — .333 ¹⁰	—	0	32	—	.12	855	5.0 14.5
3-1000Z	B SSB	3000	.240 — .670 ¹⁰	—	0	66	—	.30	1360	7.5 21.3
4CX250B ¹¹	AB1/SSB	2000	.17/.25 ¹⁰	350	—55 ¹⁰	0	0/.005 ¹⁰	0	300	6.0 2.5
	C/CW	2000	.25	250	—90	2.9	.019	.026	390	
	C/AM	1500	.20	250	—100	1.7	.02	.014	235	
4CX300A	AB1/SSB	2500 ¹⁰	.17/.25 ¹⁰	350	—55 ¹⁰	0	0/.004	0	400	6.0 2.5
	C/CW	2500 ¹⁰	.25	250	—90	2.8	.016	.025	500	
	C/AM	1500	.20	250	—100	1.7	.02	.014	235	
4CX1000A	AB1/SSB	3000	.25/.30 ¹⁰	325	—60 ¹⁰	0	.002/.035	0	1680	6.0 10.5
4-55A	AB1/SSB	3000	.015/.055 ¹⁰	360	—85 ¹⁰	0	0/.006	0	130	6.0 3.5
	C/CW	3000	.112	250	—105	1.6	.022	.009	270	
	C/AM	2500	.102	250	—150	3.1	.026	.013	210	
4-125A	AB1/SSB	3000	.03/.105 ¹⁰	510	—95 ¹⁰	0	0/.006	0	200	5.0 6.5
	B/SSB ¹¹	3000	.02/.115 ¹⁰	0	0	16	0/.03	0/.055	240	
	C/CW	3000	.167	380	—150	2.5	.03	.009	375	
	C/AM	2500	.152	350	—210	3.3	.03	.009	300	
4-250A	AB1/SSB	3000	.055/.21	600	—110 ¹⁰	0	0/.012	0	400	5.0 14.5
	C/CW	3000	.345	500	—180	2.8	.06	.01	800	
	C/AM	3000	.225	400	—310	3.2	.03	.009	510	
4-400A	AB1/SSB	3000	.09/.30 ¹⁰	810	—140 ¹⁰	0	0/.018	0	500	5.0 14.5
	B/SSB ¹⁰	3000	.07/.30 ¹⁰	0	0	40	0/.055	0/.10	520	
	C/CW	3000	.35	500	—220	6.1	.046	.019	800	
	C/AM	3000	.275	500	—220	3.5	.026	.012	630	
4-1000A	AB1/SSB	4000	.17/.48 ¹⁰	1000	—130 ¹⁰	0	0/.04	0	1130	7.5 21.0
	B/SSB ¹¹	4000	.12/.67 ¹⁰	0	0	105	0/.06	0/.15	1870	
	C/CW	4000	.70	500	—150	12	.137	.039	2100	
	C/AM	4000	.60	500	—200	11	.132	.033	1910	
3CX100A5	C/CW ¹⁰	800	.08	—	—20	6	—	.03	27	6.3
2C38A	C/AM ¹¹	600	.065	—	—16	5	—	.035	16	1.0

¹⁰ Ratings also apply to 4X250B.

¹¹ Ratings apply to 4-250A within plate dissipation limitation.

¹² Zero signal and maximum signal dc current.

¹³ Grid and screen grounded, cathode driven.

¹⁴ Adjust to give stated zero-signal plate current.

¹⁵ For operation below 250 Mc only.

¹⁶ At 500 Mc.

Above you see popular Eimac tube types suitable for professional and ham transmitters. Remember this chart when you need a tube. And remember the name Eimac. It means power. Quality. Dependability. For Eimac has more know-how, more experience with power tubes than any other manufacturer. For further

information you are invited to contact our offices at the addresses shown below.



varian PTY LTD
electron tube and device group
38 oxley street/crows nest/ nsw 2065/43 0673
679 springvale rd/nth springvale/vic 3170/560 6211

COMMENT:

A VK HI IN THE SKY

Don't brag; don't appear patronising; and let me check your spelling. That was the Editor's advice to me before I wrote my first Federal Comment.

But this time we are going to brag—we've certainly got something to brag about! With any luck, shortly after this issue is published, Australis Oscar 5 will be launched! (That's why we have the special cover for this issue.)

The four Amateur Satellites launched to date have all been built in the

United States. The fifth to be launched was designed and built in Australia. That is something to brag about! It represents a tremendous achievement for the many people involved; in particular the W.I.A. Project Australis Group.

The package has passed its sophisticated and lengthy pre-launch tests. It has "qualified" to be launched! Now, all we have to hope is that the launch is successful.

Whatever happens now cannot take away any of the credit that belongs to the group that have built Australis Oscar 5.

We can all be proud of this group of Australian Amateurs. Their achievement is something that we can all share by observing the satellite. But to them must be given the credit; to the W.I.A. Project Australis Group we say "Good luck and congratulations!"

NOVICE LICENSING

Between 1959 and 1968 it was the policy of the Wireless Institute of Australia to advocate a form a Novice licence system in this country. In detail, the following was the specific proposal advanced by the Institute:

- Morse code test of 5 words per minute.
- Elementary examination in radio theory and P.M.G. Regulations at a lower standard than that required for A.O.C.P.
- Operation to be allowed on the 3.5, 27 and 28 Mc. bands using c.w. only and crystal control.
- Power input maximum of ten watts.
- The A.O.C.P. exam. must be taken by the end of 12 months. The licence is not to be renewable except at the discretion of the Postmaster General's Department.

Attempts to persuade the Australian Administration to introduce such a system had always met with failure—which, in itself, is of course no reason for abandoning a policy. However, at the 1968 Federal Convention, the Divisions decided, through the Federal Council, that we, as an organisation, should no longer advocate the issue of a Novice licence by our Administration.

It was obvious that, despite the result, the issue was still an open one. In fact, three Divisions voted in favour of the change, two against and one abstained. Two factors that may have played some part in the change of policy were the reduction by the Australian Administration of the code standard for Amateur licensees from 14 words per minute to 10 words per minute and the lowering of the age limit at which an Amateur licence could be held.

The last nine months has seen a much revived interest in Novice licensing. Many people, some deeply involved in the Youth Radio Club Scheme, have drawn attention to the Institute's present policy, both in our

own journal and in other journals. "Amateur Radio" has received a number of letters to the Editor on this topic and perhaps significantly, not one has opposed the concept of Novice licensing. This interest has led the Federal Executive to the view that the Federal Council should again review the Institute's policy towards Novice licensing. Accordingly, it will propose the appropriate motion at the next Federal Convention. This is not to say that the Executive is advocating a change; on this matter the Executive simply raises the issue, but at least at this time, makes no recommendation to the Federal Council. I have referred to this matter at this early stage in a Federal Comment because a Novice licensing system will affect all Amateurs. By raising the issue at an early stage, I hope that all Divisions will be able to obtain the views of their members well before the Federal Convention. I hope that all Amateurs give some thought to this undoubtedly difficult question.

The arguments advanced by those for and against a Novice licensing system are fairly well known. Those in favour say that through this means we will attract new Amateurs to our ranks that we would not have otherwise attracted; that the Novice licence is particularly suitable for young people where some practical experience, particularly within the framework of the Youth Radio Club scheme is the best training. Those in favour also rely on the fact that other countries (apart from the U.S.A.) issue such a licence, apparently quite successfully.

Those opposed to a Novice licence system argue that the evidence does not support the contention that people who become Amateurs would not have become Amateurs in any event; that limited frequency band allocations to licensees with severely limited privileges create "ghettos of the underprivileged" where novices lead each other into bad operating habits; that the standard in Australia for the Full

licence is such that with application, anybody can attain it; that the Novice licence creates an underprivileged minority which is not in the best interests of Amateur Radio.

I do not pretend that the points I have mentioned are the only points for and against a Novice licence—they are not. Nor do I pretend that the points I have mentioned are necessarily the best points that either side would raise. I have quoted them as an example of the sort of issues that are raised by this question. One does not have to look far before one finds the arguments, particularly those in favour of a Novice licence, presented very ably indeed. I urge all Divisional Councils and all members to give this matter serious consideration before the 1970 Federal Convention. I hope that this matter will be a topic at least at one general meeting in each Division before Easter 1970.

But please do not only ask the question, "Should we have a Novice licence?"—do not assume that if the Institute answers that question, "Yes," that the Institute must necessarily have to advocate the form of licence it previously advocated, which is quoted above. If one concludes that we should have a Novice licence, then I think one should ask the question, "In what form do we want a Novice licence?" Indeed, it may well be easier to decide the first question after one has given some consideration at least to the second question. Open discussion on this sort of topic is, I believe, essential and one of the things that the Institute is all about. Don't be a fence sitter. Let your Council know what you think. Give your Federal Councillor any material that you think may be of assistance to him.

Whatever the result of a review of this question at the Federal Convention, I think that the criteria to be applied in judging the issue is clear. What is in the best interests of Amateur Radio? What do you think?

—Michael J. Owen, VK3KJ,
Federal President, W.I.A.

SINCE the introduction of the 146 Mc f.m. net frequencies to this country, many Amateurs have come to realise the advantages that frequency modulation provides. However, many Amateurs have only a rather sketchy knowledge of the processes involved in the frequency modulation system. It is the purpose of this article to discuss some fundamental aspects of the f.m. system.

DEVIATION

Everyone is aware of the process involved when an a.m. signal is produced. If the modulating signal is, say, 1 Kc., two sidebands, one at carrier frequency minus 1 Kc. (lower sideband, l.s.b.) and the other at carrier frequency plus 1 Kc. (upper sideband, u.s.b.) are produced. The total power in the sidebands is half the carrier power for 100% modulation (see Fig. 1a).

When a frequency modulated signal is produced with 1 Kc. modulating frequency, sidebands are produced at 1 Kc. intervals to infinity (see Fig. 1b).

However, beyond a certain point the amount of power contained in higher order sidebands is insignificant. The number of significant sidebands and the amount of power transmitted in them can be determined using Bessel functions. Two Bessel function charts are shown in Figs. 2a and 2b.

There are several points to note with reference to Fig. 1b:—

THE F.M. SYSTEM

R. F. DANNECKER,* VK4ZFD

- The carrier power diminishes during modulation.
- The energy taken from the carrier goes into the sidebands—greater amplitude of modulating signal produces more energy in the sidebands.
- One or more sidebands can contain more power than the carrier.

A small amplitude audio modulating signal of frequency 1 Kc. may produce sidebands as shown in Fig. 3a. If the amplitude is increased, the frequency spectrum of the signal may change to that shown in Fig. 3b. The signal in Fig. 3b has greater deviation than that in Fig. 3a.

A signal modulated with a 1 Kc. tone with 10 significant sidebands requires a total bandwidth of 20 Kc., while a 100 cycle tone giving rise to 10 significant sidebands requires a total bandwidth of 2 Kc.

The bandwidth required for a signal therefore depends on:

- The intensity of the modulating signal.
- The frequency of this signal.

The modulation index of a frequency modulated signal is defined as:

$$\text{modulation index} = \frac{\text{Deviation of F.M. Carrier}}{\text{Audio Freq. producing this Deviation.}}$$

For a maximum carrier shift of (\pm) 15 Kc. and a highest modulating frequency of 3 Kc., the modulation index = $15 \div 3 = 5$.

From Fig. 2a we see that there are eight significant sidebands in this signal, i.e. although the carrier has shifted only (\pm) 15 Kc., significant sidebands have been produced to $8 \times 3 = (\pm) 24$ Kc.

The relative amplitudes of the sideband sets are obtained from Fig. 2b and are shown in Fig. 4 applied to a carrier aerial current of 9.0 amperes.




Note that although the carrier is never shifted beyond (\pm) 15 Kc., significant sidebands are produced beyond this limit. Hence the seemingly wide spacing between f.m. channels.

Note also that for a modulation index less than 0.4, only two significant sidebands are produced. A modulation index of 0.4 with an upper audio limit of 3 Kc. corresponds to a carrier deviation of (\pm) 1.2 Kc. (see Fig. 5).

PHASE MODULATION

Consider an audio signal modulating a carrier such that the phase of the carrier is changed corresponding to change in the amplitude of the modulating signal. This is shown in Fig. 6a relative to a reference carrier whose phase is constant. An alternative representation in terms of rotating phasors is shown in Fig. 6b where OB is the reference carrier and OA is the phase modulated signal.

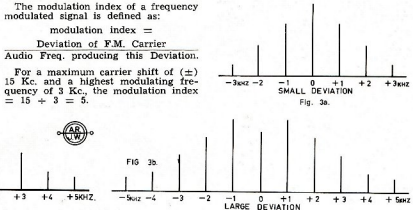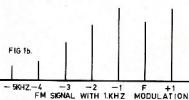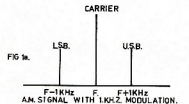Actually, in Fig. 6b, OA is rotating at angular frequency ω , while the phase varies, relatively, very slowly. Consider now the change in vector OA in going from (i) to (ii) and (iv) to (v) in Fig. 6b. In the first case OA must speed up to go from position (1) to



Modulation Index	Number of Significant Sidebands Above Carrier	Below Carrier	Bandwidth Required
0.01	1	1	2f
0.05	1	1	2f
0.20	1	1	2f
0.40	1	1	2f
0.50	2	2	4f
1.00	3	3	6f
4.00	7	7	14f
5.00	8	8	16f
7.00	10	10	20f
10.00	14	14	28f

Modulation Index	1st Set of Sidebands Value	2nd Set	3rd Set	4th Set	5th Set	6th Set	7th Set	8th Set	9th Set	10th Set	11th Set	12th Set	13th Set	14th Set
0.01	1.000	—	—	—	—	—	—	—	—	—	—	—	—	—
0.01	1.600	0.005	—	—	—	—	—	—	—	—	—	—	—	—
0.05	.9994	.025	—	—	—	—	—	—	—	—	—	—	—	—
0.20	.9900	.0595	—	—	—	—	—	—	—	—	—	—	—	—
1.00	.7652	.4401	.1149	.0320	—	—	—	—	—	—	—	—	—	—
2.00	.2239	.5767	.3528	.1289	.0341	—	—	—	—	—	—	—	—	—
4.00	-.3971	-.0661	.3641	.4302	.2611	.1321	.0491	.0152	—	—	—	—	—	—
5.00	-.1776	-.3276	.0466	.3648	.3912	.2611	.1310	.0534	.0184	—	—	—	—	—
7.00	-.3001	-.0047	-.3014	-.1876	.1578	.3478	.3392	.2336	.1280	.0589	.0235	—	—	—
10.00	-.2459	.0435	.2546	.0384	-.2196	-.2341	.0145	.2167	.3179	.2919	.2075	.1231	.0534	.0290

Note: f equals frequency of audio signal.
Fig. 2a.—Bessel Function Chart (1)

Note: Where blank spaces are indicated the values of the sidebands are insignificant.
Fig. 2b.—Bessel Function Chart (2).

position (2), in the second case OA must slow down to go from position (1) to position (3). This speeding up corresponds to an increase in frequency of the carrier represented by OA and the slowing down corresponds to a decrease in carrier frequency.

Each time the carrier phasor wobbles back and forth to reach the new phase positions dictated by the audio modulation, we find the frequency also changes in order to have the phasors reach the new positions. Note, however, that over the whole audio cycle, the average frequency of the carrier represented by OA is constant.

In producing phase modulation of the carrier we have in fact produced indirect f.m. What we are doing is adding sufficient change either positive or negative to a fixed frequency to permit the carrier to reach the desired phase position. In "pure" f.m. the carrier frequency itself is directly affected and shifted in response to the modulating voltage.

FACTORS AFFECTING INDIRECT F.M.

The amount of indirect f.m. produced depends on the extent of phase shift and the frequency of the modulating audio signal. The extent of indirect f.m. produced varies directly with both the frequency and maximum phase shift of the carrier.

In direct f.m. the value of the carrier itself swings between its maximum limits. The carrier is shifted directly by the modulation. In indirect f.m. (from p.m.) the carrier is not actually shifted by the modulation. Rather, the effect of the phase shifts is to either add to or subtract frequency variations from a fixed carrier.

Sideband Set	Amplitude (Amps.)	Power (Arbitrary)
Carrier	1.598	2.50
1st Set	2.948	8.70
2nd	0.419	0.175
3rd	3.283	10.80
4th	3.521	12.40
5th	2.350	5.52
6th	1.179	1.39
7th	0.481	0.231
8th	0.166	0.0276

Fig. 4.—Power in Sidebands

INTERFERENCE

Consider two carrier waves slightly different in amplitude and frequency. The resultant of these two waves is shown in Fig. 7. There are two types of variation in this signal as compared to carrier 1. They are: (1) amplitude, (2) phase.

In a.m. systems type (1) produces beat frequencies (e.g. 10 Kc. whistle).

In f.m. systems type (1) is eliminated by limiters in the receiver, but type (2) is still present at the detector. Note that this phase modulation produces indirect f.m. With a 2:1 ratio of desired to unwanted signals, a maximum phase shift of 30 degrees is produced.

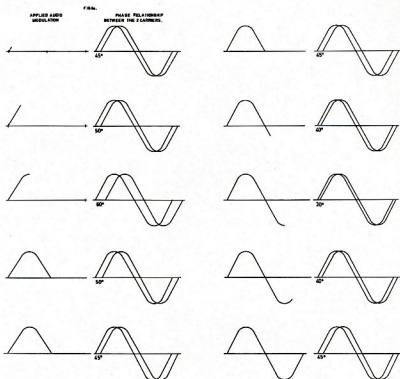


Fig. 6a.—A simplified illustration of Phase Modulation.

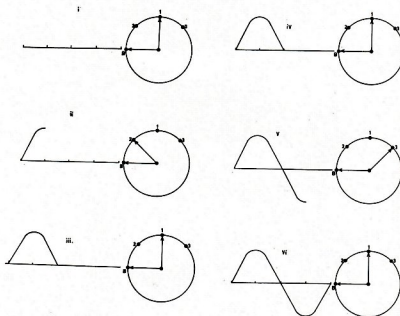



Fig. 6b.

The indirect f.m. cannot be eliminated, but in wideband f.m. systems it can be minimised.

As noted before, the indirect f.m. is directly proportional to the modulation frequency (in cycles) and the maximum phase angle (in radians) of carrier shift.

Now suppose that the interfering signal differs by 1000 cycles from the desired signal and is only half as strong as the desired signal. As noted before, a maximum phase shift of 30 degrees (approx. 0.5 radians) in the desired signal will be produced. The frequency shift (indirect f.m. produced) in the desired signal is in fact 1000×0.5 or 500 cycles. The shift is periodically above and below the average frequency of the stronger signal. The frequency variations shift at a rate of 1000 times a second (1000 cycles mod. signal).

FIG 5.

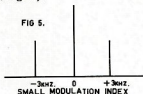

If the ordinary f.m. signal is deviated to (\pm) 15 Kc, then the (\pm) 500 cycles produced by the interfering signal produces an audio signal greatly smaller than the desired audio signal. For a S/N ratio of 10:1 this effect is even more marked. Thus the wideband f.m. completely swamps the small indirect f.m. developed from the interference. Herein lies the interference reduction power of f.m.

Note that if the two signals are of the same frequency, no interfering indirect f.m. is produced and the greater the frequency separation of the two signals the greater the amount of interference produced. However, the amplitude will be reduced by the bandpass characteristics of the receiver.

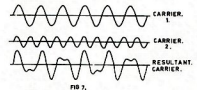


FIG 7.—The combination of two carriers to form a resultant which is amplitude and phase-modulated.

DOMINATION BY THE STRONGER SIGNAL

When two signals are comparable in amplitude, the moment one signal becomes even a trifle stronger, the response changes and the stronger signal assumes noticeable control. The process is complete when the ratio reaches the 2:1 point. (For a comparable amount of interference in an a.m. system, a ratio of 100:1 is required.)

Consider two signals of nearly equal amplitude and only slightly different frequency (see Fig. 8).

Let 1 be the stronger signal, 2 be the interfering signal and R be the

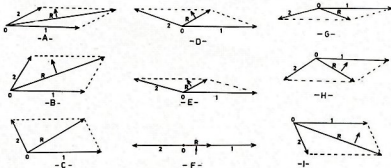


Fig. 8.—The amplitude and phase variation of a resultant (R) carrier due to the interaction of two signals. The small arrows on R indicate whether its phase (with respect to the desired signal, 1) is going in a positive or negative direction.

resultant carrier due to these two signals. As 2 rotates around relative to 1 (different in frequency), R changes greatly in phase but its average frequency is still that of 1, the stronger signal. Hence by bringing the two signals close in amplitude we have produced more phase modulation in the resultant phasor R, but R still follows signal 1, so we hear signal 1 but with some distortion produced by the indirect f.m. caused by signal 2 interacting with 1. If 2 was stronger than 1, then the phasor R would follow signal 2, hence the sharp transition from one signal to the other and this is why the predominant signal assumes control in f.m. systems.

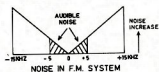


FIG 9a.

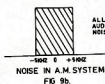


FIG 9b.

NOISE

Consider random noise in the receiver. Interactions between random noise voltages and the carrier also interactions between the random noise voltages produces:

- (1) Amplitude modulation of the carrier;
- (2) Phase modulation (and thus indirect f.m.) of the carrier.

The amplitude variations are eliminated in the limiters but the phase variations (indirect f.m.) still result in noise.

The amount of indirect f.m. (i.e. noise) is proportional to the frequency difference between the carrier and each random noise voltage, i.e. zero at carrier frequency and increasing directly with increase in bandwidth (see Fig. 9a). Above 5 Kc. we have inaudible noise (considering the response of receiver audio systems). The comparable

"noise spectrum" for an a.m. system is shown in Fig. 9b. Note the greater improvement in the amount of noise in the f.m. receiver compared to an a.m. receiver. This can be shown mathematically to be 18.75 decibels or a S/N voltage ratio of 8.65:1.

Let us now consider the effect of reducing the modulation index of the f.m. system. Figs. 10a to 10c show successive reductions in modulation index until in 10c, with a modulation index of 1, i.e. a comparable bandwidth to the a.m. system, the S/N ratio improvement of f.m. over a.m. is 4.1875 decibels. Hence the importance of obtaining the highest modulation index possible.

PRE-EMPHASIS AND DE-EMPHASIS

It is well known that most of the energy of a voice modulated transmission is contained at the lower audio frequencies, i.e. up to 3 Kc. In addition

(Continued on Page 24)

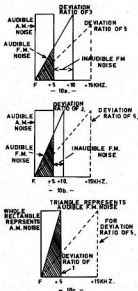


Fig. 10.—Further comparisons between the noise in A.M. and F.M. systems with various F.M. deviation ratios.

Sideband the Expensive Way (how to avoid it)

RODNEY CHAMPNESS,* VK3UG

IT is not uncommon to hear on the air and by other means of some Amateur who has just blown up his nice new Spurious Signal Breather transceiver. What happened? Well it seems that the final tubes melted into a molten mess inside the "well" ventilated p.a. cage. Why did this happen? What are the cures? That is what this article hopes to bring to your notice.

Things all started rather slowly, and is a progression of thoughts and realisations over the three years that I have been on sideband. There are a number of things that I will bring to light, that many s.s.b. operators and commercial equipment operators, in particular, seem to ignore. They think either the manufacturer has solved all their problems, or that they, through ignorance or pure laziness and lack of an inquiring mind, have not bothered to think about it.

First, I will start with your tabletop transceiver, which, according to manufacturer's literature, runs 500w. p.e.p. input to a pair of, say, 6KD6 valves. Wonderful what you can get out of these colour t.v. line sweep valves. Wonderful how many watts per cubic inch these miniature rigs run to. Funny thing, though, the case of the transceiver is almost too hot to leave your hand on for long. Ever tried touching the p.a. final valves when they are just running with class AB1 bias and not being driven? You could boil water on them.

The normal p.a. tube in the majority of s.s.b. rigs is run with a standing current which is very little below the allowable dissipation rating of the valve. Then you go and talk the thing up to some astronomic current, not even marked on some popular rigs. Boy, are you then exceeding the dissipation ratings, and how!

As an example, take a 6DQ5. This will run in class AB1 maximum of 750 volts and 280 mA., which works out to a d.c. input of 210 watts d.c. I believe some rigs do run these valves at these figures in AB1 in the c.w. mode. Allowing for a 50% duty cycle still in excess of a 100 watts and the 6DQ5 has only a 32 watt dissipation rating. Class AB1 is rarely much more efficient than about 55%, so this would mean that the 6DQ5 would be dissipating about 47 watts, which is about 50% above maximum ratings. Now sideband runs, according to many, a duty factor of about 30%, so in this case the valve would be just inside its ratings—or would it? No, it is not, as its normal standing current is nearly the maximum dissipation ratings. So once again you are exceeding the ratings unless you use VOX.

Now many loud mouthed Amateurs believe that the rig should read in p.a. current, nearly as much as it should

in the c.w. position with the key down. Wow, have you heard their signals? They are the sort of signal that can be tuned as splatter from one end of the band to the other, and I'm not exaggerating, ask Ron Fisher, VK3OM. We experienced a "perfect" example of this one night on 80 metres. To accomplish this high p.a. reading, the audio is turned up, the microphone bellowed into, a compressor and/or pre-amp. fitted and hope to blaze the a.l.c. takes care of this abuse.

The a.l.c. is not designed to act as a speech compressor but more really as an overdrive preventer and splatter preventer. The a.l.c. can only tolerate a certain amount of overdrive, then in most cases glorious splatter emerges. It must also be remembered that there must also be a correct ratio of carrier to audio in the balanced modulator. The audio is considerably weaker, usually by a ratio of about 10:1. If, through your compressor, pre-amp, you decrease this ratio up comes your distortion almost straight away. Once there is distortion in the signal, nothing you can do will effectively get rid of it.

Take pride in the quality of your signal, not how many db. over S9 it is. So now it can be seen that by driving your p.a. tubes hard, through either calculated commercial over-rating, or breathing heavily into the microphone system, expensive damage can be done to the p.a. valves. In these small transceivers and transmitters the ventilation is far from adequate, so still more de-rating of the valves is required. I have extreme doubts that any commercially made Amateur transceiver would come anywhere near the reliability in transmitting time, that a commercial service


transmitter would or, for that matter, the old a.m. rig you threw out, when you got this new s.s.b. rig. The 807 in it is still probably the original, and it was still running at least 80% of its new performance.

Well, having dispensed with the preceding causes of poor s.s.b. signals and causes of red hot p.a. tubes, I'll pass onto another perhaps more subtle cause of trouble in s.s.b. transceivers and transmitters.

Many months ago I became plagued with a mysterious sudden increase in p.a. current in my Yaesu FL200B transmitter whilst I was talking. I would find that my resting p.a. current would suddenly jump from 60 mA. to about 250 mA. The only way to get it back to normal was to release the transmit button. What was wrong? All sorts of thoughts ran through my mind from grid-cathode shorts, to bias failure, grid emission, ad nauseum.

At about the same time I was also getting intermittent reports of something wrong with my signal. Eventually Ron VK3OM said to me that my signal was f.m.-ing. Horrors, well what could cause this. Variation in v.f.o. h.t. voltage? Yes, this proved to be the answer, but why? The Yaesu uses a rather sophisticated h.t. regulation system which feeds not only the v.f.o. but also the p.a. screens. What had occurred was that I had tuned the rig up ah la book to give the required p.a. current and general expected output level. The way I had loaded the tx was such that the screen current was much higher than it should have been, due to rather light loading of the p.a.

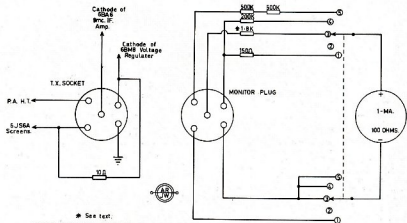To get the p.a. plate current up, the drive was increased. I went onto speech,



YAESU FL200B TX MONITOR.

Switch Position	
1—Screen current.	0-25 mA.
2—OFF.	
3—A.L.C.	
4—Regulated H.T.	0-200 Volts.
5—P.A. H.T.	0-1000 Volts.

* 24 O'Dowds Road, Warragul, Vic., 3820.

then on speech peaks the screen current exceeded the c.w. level, so causing the voltage regulator to be overdriven, so loss of regulation. The moment regulation is lost the voltage tends to climb as the regulator requires a higher ignition voltage than maintaining voltage. Speech peak over, the voltage rises as current drain is reduced, but then due to higher voltage on the screens, they draw more current and so do the plates, due to having a much higher screen voltage. The regulator is unable to regain regulation so this destructive situation prevails.

The solution to this problem is fairly obvious. I must load the transmitter so that the screen current is much more reasonable. How can I tell that this current is about right? There is no meter on the Yaesu or to my knowledge any other s.s.b. rig. Anyone who has done some reading about s.s.b. will perhaps vaguely remember something about screen current being observed for tuning a s.s.b. rig final. High s.w.r. readings and slap-happy methods of tuning will cause screen currents to be dangerously high for the tubes. In my experience in commercial s.s.b. transmitting equipment up to about 3kw, d.c. input, this proved quite a problem with reactive aerials. A lightly loaded final, whether s.s.b. or a.m., can almost be considered as being a final in which the plate circuit is open circuit and the screen has the doubtful pleasure of acting as the plate. It attempts to draw currents such as the plate would draw, but due to its structure its dissipation is low and therefore grossly exceeded. The screen gets red, then white hot, and then disintegrates. Exit the p.a.

Notice in the preceding paragraph that I jumped the a.m. and s.s.b. finals in together, in regard to light loading and the effects on the screens. Now you will say if this is so, how come I didn't blow my old 807 up with light loading? The reason is quite simple. Consider the old a.m. final, an 807, with 600 volts on the plate and the screen running at 300 volts fed through a 37,500 ohm resistor from the 600 volt supply. The screen current is 8 mA. Now lightly load the final and the screen attempts to draw say 16 mA., the screen voltage will be a big fat zero. So in the case of the lightly loaded a.m. final, the screen current cannot rise much, as the voltage will be reduced to the screen very drastically. The screen is thereby fairly well protected.

Now the case of your nice new s.s.b. final. The situation here is much different. The screen voltage must be regulated for the linear to function in a linear manner. Now with the final lightly loaded, the screen current does rise to this level of 16 mA., using the same set of figures as stated for the a.m. rig with the exception of no screen resistor. The screen voltage is regulated and stays the same as with normal loading. We'll load the final more lightly again, more screen current and less plate current. We're well on the way to destroying the final p.a. screen grids. We've already got a signal that isn't all it should be in the way of quality.

Well I hope from the preceding information that I have perhaps helped to clear some of the fog which seems to descend when we change from a.m. to s.s.b. The things which were of little importance, so we thought, in the days of a.m. are quite important in regard to proper operation of s.s.b.

Before I finish this article, I will just show you how screen current varies as a function of plate current in my Yaesu tx, and will describe what I call my "Tx Monitor". This device is just a meter with shunts and multipliers so that I can monitor screen current, regulated h.t., p.a. h.t., and a.l.c. With 300 mA. h.t. current drawn by the p.a., I find that loading the final so that a screen current of 8 mA. is drawn gives best results, with my FL200B tx.

The following table should give you some idea of how screen current escalates with increased drive levels, such as when the gain is turned up full bore (p.a. tune and loading left untouched):

PA Current	Screen Current CW	Screen Current SSB
100 mA.	0.5 mA.	Approx.
150 mA.	1 mA.	double c.w.
200 mA.	2 mA.	reading for
250 mA.	4 mA.	same p.a.
300 mA.	8 mA.	current.

Table for two 6JS6A valves in parallel in Yaesu Musen FL200B.

"TX MONITOR"

Now to the "Tx Monitor". This was built into a plastic case 8" x 3 1/2" x 2 1/2", available from "A.R." advertiser. The meter is a 1 mA. movement of the MO-65 style. The switch was an ordinary Oak MSP 2-pole 5-position single bank switch. The unit is attached via a five-core cable to a miniature 5-pin plug which fits a miniature 5-pin Mc-

Murdo socket on the rear apron of my transmitter.

The transmitter wiring modifications are self evident from the diagram. The metering ranges are as follows: (1) screen current, 0-25 mA.; (2) no connection; (3) a.l.c. (no levels marked); (4) regulated screen voltage, 0-200v. (normal 150 volts); (5) p.a. h.t., 0-1000 volts (normal 600v.).

The 150 ohm resistor presupposes that the meter resistance is 100 ohms, so making up a total of 250 ohms. The 1.8K ohm resistor is subject to experiment to get full scale reading in the a.l.c. position with no modulation. It may need to be higher or lower in value. Unless you use 1% resistors in all positions, you may need to play around with the exact values to get correct readings.

This is shown as made to suit my Yaesu tx but could be easily adapted to suit any transceiver or transmitter. I find this little unit to be an extremely handy accessory to my transmitter. I would not think now of tuning the rig without monitoring both the p.a. plate current, or actually cathode current, and separately the screen current. I know a little more with this monitor about what is going on inside and find this most rewarding, and I might add I haven't blown up any p.a. valves yet. This unit is part of my insurance that I don't.

I would recommend for your reading the various articles that have been in the s.s.b. notes which appeared a few years back. Most were written by VK5NN. A recent article in "A.R.", which bears close study is the one appearing towards the end of 1968 by VK2AOU. This gives excellent data for anyone wanting to build or just perhaps to understand a little more about this mysterious mode many use, called s.s.b. Mysterious, because few really understand much about its finer points, and I'm one of those who has got a lot to learn yet.

SWAN NEWS LETTER

Swan Electronics are now rapidly expanding their operations into other products and to further this end they recently purchased the well known antenna company of HORNET ANTENNAS.

This now gives Swan a full range of very sophisticated antennas for both commercial and amateur operation. These antennas are now known as Swan Hornet antenna and cover multiband beams, both full sized and shortened; trapped vertical, all band; trapped dipole, and mobile whip types.

As the Swan factory distributor for Australia, W.F.S. Electronic Supply Co. will shortly have stocks of these very fine antennas; the following types will be the first to be available:

TB1000-4	FOUR ELEMENT TRIBAND BEAM	1000 WATTS
TB1000-3	THREE ELEMENT TRIBAND BEAM	1000 WATTS
TB750-3	THREE ELEMENT TRIBAND BEAM	750 WATTS

W.F.S. ELECTRONIC SUPPLY CO.

12 BOWDEN ST., NORTH PARRAMATTA, N.S.W., 2151. Ph. 630-1621

also SWAN SERVICE, 14 Glebe Street, Edgecliffe, N.S.W., 2027. Phone 32-5465

Conversion of Circuit Diagrams to Veroboard, Tag-Board and Printed Circuit Layout*

A. T. CAMPBELL, G3PEQ

WE have all had the frustration of wiring up a circuit from a diagram, painfully trying to avoid errors and to miss nothing out. Then after a quick check through, the circuit has been connected to power—and it hasn't worked. Frequently more time is now spent in finding and correcting the fault than was occupied in the actual construction.

The method I am going to describe avoids all this. It enables the layout to be achieved automatically, except for printed circuit boards where a little thought is required. Checking is easy and thorough, and can be done systematically on paper without the need for poking about among a complex of wires and, according to Murphy's Law, missing the one thing one is looking for.

Normally one traces through a part of the circuit, taking the components involved one by one and connecting them, one hopes, to the right places. Let us forget all that, relegate the components to a secondary position, and concentrate on the junction points. We will illustrate this with a simple one-transistor amplifier which we will lay out for Veroboard construction.

VEROBOARD

Fig. 1 shows seven junction points, for the negative and positive lines can be considered as extended points, as shown in Fig. 2. It does not matter how we number these points, except that it is advisable to number the leads of the transistor in the same order as they emerge from the case so as to avoid twisting them, with risk of breaking off or shorting when we insert the transistor. In the diagram I have not put in the value of the components, but have lettered them in order to make reference easier in the following descriptions.

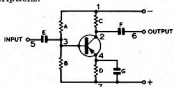


Fig. 1.—A simple amplifier.

After a little practice, you can now immediately wire up the circuit; but until experienced, it is well to go through the following stages, first laying out on paper and then checking.

On a sheet of paper, draw seven lines, numbering them from 1 to 7 to correspond with the junction points of Fig. 1 (see Fig. 3). Now proceed to draw in the components; you may do so in the literal order, A to G, to avoid

the possibility of missing any; or, if you have any spatial imagery, insert them in the order which will waste least space, which is what I have done here.

Taking then the resistor A, we note it is connected between 1 and 3. Mark clear dots on lines 1 and 3, join them with the resistor symbol and label A (in practice, of course, with the actual value). C is connected between 1 and 2 in the same way, and the capacitor F between 2 and 6. Now mark in the transistor at 2, 3 and 4, indicating either the collector or emitter; if you have labelled the transistor leads consecutively you need label nothing else

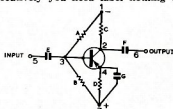


Fig. 2.—Amplifier circuit re-drawn to show positive and negative rails as points.

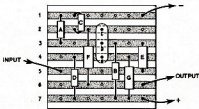


Fig. 3.—Veroboard layout of the amplifier.

because the leads will automatically come in the right place. Similarly we mark in B, D, G and E and indicate four points for the connection of input, output and power. It does not matter, of course, at which end of the lines you mark these last four points; you suit your own convenience entirely.

The layout is finished; checking must begin.

Quick Check: Count the number of components on the diagram and layout. If these do not agree, find the error. If they agree, refer to point 1. There are three connections at this point; there should be three dots on line 1. At point 2 there are three connections and again three dots; at point 3 there are four connections and should be four dots; and so on for the remaining junction points. This is a sufficient check in most circumstances, but you can, if you wish, proceed to the:

Certain Check: Consider component A; one end is connected to C and the negative line; the other to B, E and the base of the transistor. Check that

these connections actually take place in the layout diagram, and proceed to check each component in the same way; finally checking that positive and negative lines, input and output are correctly connected. If everything tallies, you cannot be wrong!

Cut a piece of Veroboard to size. Select the components required and check them thoroughly. This is a point often overlooked (through laziness!) and causes more trouble than anything else. You can spend hours looking for a wiring fault, when it is a component that is faulty, or wrong value. Resistors are easily verified with a test-meter, but if you have no method of checking capacitors, which are much more likely to be faulty, build yourself a capacity bridge; it will repay the time spent on it over and over again. Measure at least the forward and reverse resistances of the transistor diodes; but if you are using it in, say, a phase shift oscillator circuit, you must measure the gain also—a simple thing to do with a quick hook-up.

Having checked components, label the rows of Veroboard in some way to show the numbering. A strip of gummed paper may be stuck on, or a piece of Sellotape-X, or they may be marked with a reed pen or a grease pencil. Do not omit this, unless you are less fallible than I am! Now bend the leads to fit into the right holes, remembering that the vertical positioning of resistors is often a great help; clean the leads where they will make contact with the foil, bend them over, cut off, leaving about 1/8" of wire, and solder. Conclude by soldering in either pins or wires for the connections to power, input and output and mark them with a piece of gummed paper, grease crayon, or other means.

You have finished and you can't be wrong!

Now let us tackle a multi-vibrator used as an audio oscillator. The snag here is that as both transistors have a common connection to the emitter, we cannot number the leads consecutively, but we get over this by numbering the collector and base of TR1 as 2 and 3 and follow immediately with TR2 numbered 4, 5 and 6. Then the emitter of TR1 will also go to 6, the length of the leads normally being more than enough to do this. So Fig. 5 becomes the layout of Fig. 4.

In anything more complicated than these two simple circuits, one difficulty sure to occur is that the number of junction points is greater than the number of stripes of copper available. To cope with this we break a number of strips at one or more points to provide the requisite number of connections, obviously choosing strips for breaking which have only a small number of connections going to them. If

*Reprinted from "Radio Communication," July 1968.

the strips are carefully numbered on the Veroboard, no difficulty in connection can arise. If much Veroboard work is done, a spot face cutter should certainly be acquired as it saves much work and makes a good job; but if this is lacking, a 3/16" twist drill rotated in the fingers will break the strip easily and cleanly.

It may be found advisable, in order to get a leadout in a more suitable position, to break a short strip where required for the leadout and connect with link of insulated wire to the point it derives from. The same method can be adopted if the lead of TR1 is not long enough to reach to strip 6. This, and many other useful dodges will quickly be realised as soon as you have laid out and built one or two Veroboard circuits.

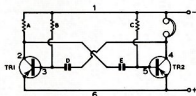


Fig. 4—A multi-vibrator as an audio oscillator.

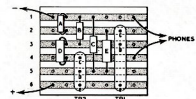


Fig. 5—Veroboard layout of the oscillator.

I was so pleased with the above method of construction that I built several dozen small and large pieces of apparatus, quite satisfied that this was the ultimate in building methods. But gradually disadvantages from the experimenter's, rather than the builder's point of view began to appear. The experimenter wishes to change components to examine the effect of varying values, and to make measurements from different points of the circuit. Neither of these is easy with Veroboard construction. For these purposes, tag-board construction has many advantages; but in my opinion, it is ungainly in appearance; one seldom has the right size of group-board available, and connecting up and checking is a tedious procedure. The last of these difficulties disappeared on a little reflection, and an adaptation of the methods used for Veroboard made layout and checking completely straightforward. How to get over the difficulty of the awkwardness of group-boards?

TAG-BOARD (OR GROUP-BOARD)

The first approach was to drill paxolin sheet to take turret tags in the required positions and thus to build up a tailor-made group-board. The result was pleasing and satisfactory, but time-consuming. The method I invariably use now is to build up my group-board with soldering pins on plain Veroboard, achieving quick construction and one

which looks really well when finished and in which the components are more securely fixed whilst at the same time they can be easily removed and changed, and measurements are quickly made from any required pin.

The most convenient board I find is the Elektrokit Chassis Plate No. 4, LK-141, obtained from Home Radio at 3/- each. These are approximately 5" x 4" and contain 40 rows of 35 holes spaced 1/10" apart. Each will provide three 20-way group-boards or half a dozen or more smaller ones. The soldering pins are sold in packets of 100, their ordering number being LK-3011. The plate is most easily cut with a pair of side-cutters; if each edge of the plate is cut with them at the required spot, the whole separates neatly.

But let us first deal with the layout, then the construction. For convenience, we will use the circuit of Fig. 1 for our design.

The first step again is to number the junctions, but this time we need pay no attention to the transistor leads, but may number them in any order we like. However, to save another diagram, we will use the same numbering already on the figure.

There are eight components, so we draw an 8-way group-board, as in Fig. 8, then draw in the symbols for the components. It will ease wiring if we group together components connected to each other, so we begin with the components associated with junction point 3, where there are four leads connected. Note that it is perfectly easy to insert another pin for the base connection of the transistor, so we do so, offsetting the base pin towards the emitter to prevent error when we come to put the transistor into circuit. The top (or bottom) ends of E, A and B are labelled with their number, 3, and the other ends will be 5, 1 and 7 respectively, and the transistor 2, 3 and 4.

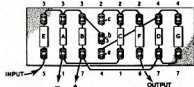


Fig. 6—The amplifier arranged for group-board.

The other components are drawn in, keeping together so far as is possible those connected to each other, and numbering the ends in the way which seems likely to need least wiring. Follow all this in Fig. 6.

The complications of wiring reduce to one simple rule: join all the corresponding numbers! I use a red pen for this, but I have no doubt it will be reproduced in black.

One thing remains to ease our work; take a piece of tracing paper and trace the tags and joining wires and then reverse the paper. This is how the wiring will appear on the back of our group-board.

Checking is as with the Veroboard. Take point 1, observe what is connected in the circuit diagram and check that they are all wired together on the tag-board. Checking each component sim-

ilarly can be done if thought necessary, but it is a work of supererogation.

Take a piece of plain Veroboard and with the fingers insert the pins as in Fig. 6. I leave one space between each pair of pins and seven spaces between the two rows, giving a width of 0.9", which is about right for 1 watt resistors and miniature capacitors, but you may, of course, modify the spacing as you wish. Having inserted the pins, take a pair of small pliers and press them in firmly, keeping the heads at a uniform height above the board.

Reverse the board and wire up. Tinned copper wire 26 s.w.g. is just right for this; it is easy to work and sufficiently rigid for there to be no danger of the loops 1 and 7 touching each other if bent away in the first place. When there appears a danger of wires touching, slip a piece of sleeving over one of them.

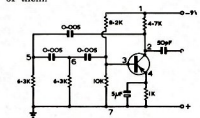


Fig. 7—A phase-shift oscillator. Unmarked units are kilohms or microfarads.

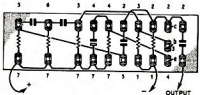


Fig. 8—Group-board layout of phase-shift oscillator.

If you are ultra-cautious, restore the board to its original position and with an ohm-meter check that the pins are connected as in Fig. 6. This should reveal any dry joints.

Nothing remains now but to check all components (yes!) and solder them into position as in Fig. 6.

The method is fool-proof—but I admit there are fools and fools!

I think one should refrain from connecting components across the board between separated tags, as is a very common practice, but there are times when a departure from this rule can be advantageous. A good example is the phase-shift oscillator, Fig. 7. Here connecting the two 0.005 uF capacitors between the ends of the resistors (see Fig. 8) is obviously economical of space, time and wiring and by allowing two spaces between tags 5, 6 and 3, instead of the usual one on the plain Veroboard, the fitting-in of the components becomes physically easy.

If you build this phase-shift oscillator, don't forget you must use a high-gain transistor to overcome the attenuation introduced by the three phase-shift circuits.

PRINTED CIRCUIT

And so we come to what many regard as the ultimate in lay-out dif-

faculty—the printed circuit. Using our methods, this involves no more difficulty than the other layouts, but does require a little thought and care in arrangement.

Turning again to our audio amplifier, Fig. 1, we first evolve the tag-board layout of Fig. 6. This obviously cannot be used as it stands for a printed circuit as two leads cross, but it is a simple matter to re-arrange them as in Fig. 9, from which is immediately derived the printed circuit of Fig. 10. Place a piece of tracing paper over Fig. 10, trace it, reverse the paper, mark through on to the copper foil of the printed circuit and you are all set for etching, drilling, etc.

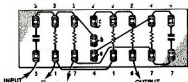


Fig. 9—The group-board wiring of the simple amplifier modified for printed circuit.

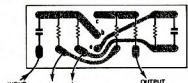


Fig. 10—Printed circuit for simple amplifier.

Similarly the circuit of the phase-shift oscillator first becomes the tag-board of Fig. 8 and is then easily transformed into the printed circuit of Fig. 11.

With a complicated circuit you may easily find that the avoidance of crossing wires involves a complicated circumambulation all over the board, or is altogether impossible. This may be sometimes cured by a simple re-arrangement of the components; but a very simple, and always certain, cure is to solder a link of insulated wire between the two points to be connected.

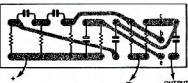


Fig. 11—Printed circuit for the phase-shift oscillator.

Using the above methods, especially the first two, I find myself much freer to experiment when an interesting circuit swims into my ken. Unless it is complicated, I can have the circuit built and working in an hour—often in half an hour. I usually confine my construction now to the tag-board method, and if the finished item is not needed to be retained, the components are easily unsoldered and ready for use again, all leads cut to the right length, tinned and ready to be soldered directly into the next bit of equipment built.

JOE

A. J. C. THOMPSON,* VK4AT

People appear to think that staid people like myself should be playing bowls instead of taking up Radio. They even ask for details of the events that led up to the decision of selecting such an unusual hobby.

Actually those circumstances occurred in my far distant youthful days. It has just been the fear of doubts being cast on my veracity that has kept me quiet for so long.

Being home from College on holidays at one time, it was rightly assumed that I knew all about electricity. It was no surprise to me that I was chosen by some vegetable-growing foreign-born citizens to explain the mysteries of an electric fence that they had recently acquired. These things were mysteries to all at that time, including myself.

Having mastered Ohms Law and the art of throwing switches, little things like electric fences would be nothing to me.

In a dignified manner I ushered the bashful foreigners into my sanctum.

In a truly professional manner I soon had the cover off.

I remembered then that our College instructor spent a lot of his time warning the unruly members of our tribe on the danger of going up in smoke if we placed our fingers here and also there.

It appeared to be quite a good take-off point. The language difficulty gave me an opportunity to air my French.

"You touchez here, you touchez there, beaucoup blue sparkies go upski, beaucoup corsepy plonk go downski."

Charlie appeared surprised at my knowledge of foreign languages, but Joe grasped eagerly at the only word that evidently he understood. He tapped his red shirt all smiles, "Blue Blue".

I patiently explained to him that it was only in France that blue was red. It was evident, at this stage, that the language business was going to be tough.

I tried a new tack. I connected up the gadget to the battery according to the instructions and off it went, tick, tick. I pointed to the little spark on the points, but they made it clear that they desired big sparks.

I remembered then that our teacher lined the whole class up, and then put a little tangle through all their fingers as we held hands. He used a little gadget that looked like this.

A couple of 6-inch nails made good handles when the bare wires were attached from the two output terminals. Joe held one and I had the other, while I held his hand to make the circuit. Before I switched it on, I decided that it was a pity to leave Charlie right out of things.

* Skyring Creek, Pomona, Qld., 4568.

After a bit of thought, I decided to improve on the College method. I could let Charlie observe the spark at the same time as Joe felt the tingle. I explained to Charlie, who evidently understood our language, that instead of holding Joe's hand, I would, instead, make the blue spark go on to his ear from my fingers. This would be at a convenient height where we could observe it easily.

All being set, I approached Joe's ear with my finger, while Charlie and I pressed close to see how far the spark would jump. Joe, with a happy smile, cocked his eyes sideways in the hope of seeing the tip of his ear at the crucial moment.

When I closed the switch things happened quickly. To our astonishment (mine was much different to Charlie's), Joe's ear disappeared upward, with Joe still attached to it. When he came down again he lay on the floor muttering.

Charlie tended him. Mystified, I asked Charlie what Joe was doing down there? Charlie shook his head: "Too much blue sparkies". Joe still muttered.

"What is he saying now, Charlie?"

"Him say him understand corsepy now. Him head hit the roof, but him feet stay on floor."

Patiently I explained to Charlie that we ourselves had seen Joe ascend and descend all in one piece. I explained that if I had been holding Joe's ear then he might quite easily have lost it.

At this stage, Joe started thrashing around.

"What is biting Joe now, Charlie?" I wanted to know.

"Him want looking glass" was the unexpected reply.

However his wants were easily supplied, but his behaviour was peculiar. Instead of looking at the bump on his head, he was examining himself all over. He even got Charlie to hold the mirror while he rolled over. He then studied his back.

Curiosity got the better of me. "What is he doing that for Charlie?" I asked. The reply explained all.

"Him very worried man. Him afraid him turn round before him head get back on."

We got Joe up and soothed down, but he would not stay. He felt all right but he thought he would just walk home.

Just after he had left, my fond parent arrived with suitable refreshments. She observed Joe's stately walk with some astonishment, then asked Charlie, "What is Joe doing walking like that? And why is he holding his head with both hands?"

Charlie's reply completely mystified her. "Him hold him head on for fear him head fall off again."

These events impressed me greatly. It was quite natural that I should take up Radio after witnessing the strange effects of such electrical gadgets.

I often wonder though if Joe took up Radio too.

HIGH VOLTAGE REGULATORS

RODNEY CHAMPNESS,* VK3UG

THE majority of high voltage regulators seem to use either the old 807 or 6AS7 valves, the first being a rather high impedance valve and the latter a rather expensive valve. There is nothing that could be called new in either of the two regulators that are described below. The first one (Fig. 1) is rather simple and as long as you can stay within the dissipation ratings of the valve currents of up to 75 mA, voltages up to 220 volts d.c. can be obtained, so varying on using series parallel banks of VR tubes for some applications.

The larger regulator (Fig. 2) can supply voltages up to 300 volts at currents up to 200 mA., and with the possibility of even being able to supply currents up to 250 to 280 mA. with the substitution of other series lossier valves.

The 6GV8 is a t.v. vertical section valve and has characteristics such that at rather low screen voltages of below 150 volts, it can draw currents up around 75 mA. without the grid approaching closer than a few volts of zero grid bias. The grid bias must at all times remain negative in this and the larger regulator, otherwise regulation ceases.

Consider the operation of the triode section first. The unregulated voltage is supplied through a $\frac{1}{2}$ meg. resistor to the plate. The grid will be at earth potential if the slider is at the earth end of the 50K pot. The NE2 neon lamp will tend to light and will assume a voltage drop somewhere about 60 volts, so the cathode of the valve will be 60 volts positive to the grid and the valve will be cut off. The pentode section will then receive positive grid voltage via the $\frac{1}{2}$ meg. resistor, causing this valve to conduct heavily, which will mean that the cathode will be about the same potential as the grid. However, this will not be the same as the unregulated h.t. as the grid current will cause a voltage drop across the $\frac{1}{2}$ meg. resistor.

If now the slider across the 50K pot. is removed from the earth end of the travel to mid travel, so that the slider is sampling about quarter of the voltage present at the pentode cathode, the regulator will now be operating. As the cathode of the triode is at about 60 volts positive, the grid will be about 55 volts positive in approximate figures and drawing a certain amount of current which will be causing the plate voltage to settle at about 200 to 215 volts, depending on the current being drawn from the regulator. This voltage is applied directly to the grid of the pentode and the cathode will assume a voltage from 5 to about 15 volts more positive, depending on current drain, so giving the pentode a negative bias of this amount. The cathode will be approximately at 220 volts due to the voltage divider arrangement in its cathode circuit. If the slider is at the

top of the pot., it will be sampling half the voltage of the output to the triode grid, which will still be at about 55 volts and so the cathode of the pentode will now assume about 110 volts positive, as its grid will be about the 100 mark, plus or minus a few volts depending on the current drain.

Now assuming the pot. is set such that an output voltage of 200 volts is obtained at 5 to 10 mA, the triode grid will be about 55 volts and the triode

requires perhaps 90 volts to ignite it, the plate voltage will not rise enough, as the pentode will still be drawing grid current because of this "new 90 volts" reference voltage causing the supply to think it has to supply 50% more output voltage. With this higher output voltage, more current is drawn by the supplied unit and more or less locks the regulator out of regulation. For this reason a zener diode reference source is preferred.

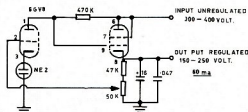


FIG. 1 60 mA. REGULATED SUPPLY.

plate pentode grid will be about 185 volts. Now the load is increased to say 60 mA., the output voltage will tend to drop, causing the voltage on the grid of the triode to drop, so causing it to conduct less and the plate voltage to rise. As the pentode grid is directly connected its grid voltage will rise or its negative bias will become less, causing the valve to conduct more and so restore the original output voltage. This output voltage can also be maintained at a constant voltage with variations in the unregulated supply voltage input.

The main things to remember with this simple supply are that the minimum difference voltage between the unregulated input, and the regulated output, should be at least 120 volts and that the current is not to exceed 75 mA. and that the output voltage is not to exceed 220 volts, unless the heater of the valve is supplied from a separate supply, as the cathode-heater maximum voltage rating is 220 volts. The plate dissipation rating of 9 watts should not be exceeded.

The resistor potentiometer in the pentode cathode circuit can be altered to suit a specific design need. The unregulated supply input will determine to a certain extent the output voltage. The NE2 neon can be replaced with a zener diode of about $\frac{1}{2}$ watt rating, 60 volts, or nearest convenient voltage. Using a zener in the cathode will mean that the output voltage will drop should the current drain be such as to cause the pentode to draw grid current. As soon as the excess load is removed, the supply will resume normal operation.

With the neon lamp, however, this is not the same. If the pentode draws grid current, the neon will drop out of conduction and the voltage drops. If the load isn't dropped much below overload, the voltage will then go high by perhaps 40 to 50 volts. As the neon

As a point of interest, f.m. caused on one variety of s.s.b. transmitter is from this reason. The transmitter is incorrectly tuned, causing excess screen current to be drawn by the screen on speech, the regulator goes out of regulation, sometimes staying out as the screen draws high standing current when the voltage jumps to 200 volts from 150 volts. The v.f.o. is on the same 150 volt line, so is it any wonder that the v.f.o. jumps around in frequency. The regulator doesn't always lock out and the result is a beaut case

TECHNICAL ARTICLES

Readers are requested to submit articles for publication in "A.R.," in particular constructional articles, photographs of stations and gear, together with articles suitable for beginners, are required.

Manuscripts should preferably be typewritten but if handwritten please double space the writing. Drawings will be done by "A.R." staff.

Photographs will be returned if the sender's name and address is shown on the back of each photograph submitted.

Please address all articles to the
EDITOR "A.R."
P.O. BOX 36,
EAST MELBOURNE,
VICTORIA, 3002.

* 24 O'Dowds Road, Werragul, Vic., 3820.

of f.m. How to cure this? Tune the transmitter properly.

Now we turn to the larger of the two supplies (Fig. 2). This is designed around 1 v. line output valves such as the 6CM5 in this instance, although I feel a 6DQ6 could be better due to higher plate dissipation. The reason for the choice of these particular valves in preference to the old and trusty 807 is simple. The screen of the series loss is virtually connected to the plate, the 807 requires about 300 volts for it to draw reasonable current, but the likes of the 6CM5 require only 100 volts or a little more between plate/screen and cathode to draw identical currents. This simply means that with an 807 as the series loss, an unregulated input of about 600 volts will be needed for a 300 volt output, whereas with the 6CM5 a 400 volt unregulated supply could be sufficient. This is considerably more economical on power and cost of the necessary transformer iron.

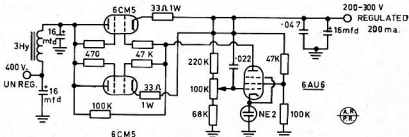


FIG. 2 200 Ma. REGULATED SUPPLY.

There are a few noticeable differences between this larger supply and the smaller one. It will be noticed that the screen and grid of both series loss 6CM5 valves have stoppers in their leads. This, strange as it may seem, is absolutely essential in many cases, particularly when two valves are paralleled. Even though this is a supposedly d.c. circuit, these valves take off very effectively at all sorts of odd frequencies, up to at least the 14 Mc. band, and the regulation just doesn't work. The 33 ohm resistors in the cathodes of the two series lossers is for current equalisation, so that both valves take approximately the same current. Without these resistors, one slightly seedy 6CM5 would let its fellow take most of the current and go red in the face.

The 0.022 uF capacitor from regulated output to regulator control grid (6AU6) is designed to inject some hum from the regulated output into the regulator circuit to improve output voltage filtering. Another way of achieving the same thing is to break the 100K ohm resistor between the 6CM5 plates and the 6AU6 plate into two 47K ohm resistors with an 8 uF capacitor connected to the junction of the two resistors and the other end to earth.

The only other point to note is that for 6CM5 valves, or whatever valves of this type used, a separate filament supply will be necessary that is not tied to ground, as the heater-cathode rating of these valves is only of the order

of 100 volts, so be warned! There is no worry in regard to the 6AU6 cathode-heater rating as the voltage is only about 60 volts across these two, which is well below the allowable maximum.

Layout of parts for the supply is not critical, except to make sure the loss valves have adequate ventilation.

Considering that the 6CM5 valves are only rated at 13 watts each, the estimated current drains must be calculated so that the valves are not ruined. With 400 volts input and 300 volts output, we have a drop of 100 volts. This means that W (watts) = I (current) \times E (volts); in this case W is 26, E 100, therefore I is $26 \div 100 = 260$ mA. maximum current. With an output voltage of 200, however, $I = 26 \div 200 = 130$ mA. maximum current. In between voltages will mean different output currents.

Using 6DQ6A valves which have a 5 watt higher dissipation, will mean at the lower voltages more current can be drawn. In the case of 200 volt out-

put, the current maximum is 180 mA., although I feel these particular valves are rather conservatively rated and you may, with experimentation, just to see how they take it, try them at 200 mA. on 200 volts. I've seen some of these 6DQ6A valves take a thrashing in s.s.b. linears, and have run personally 80 watts c.w. to one without an ounce of trouble. This was with the unit running into dummy load for minutes on end with the key down and not a sign of red gills. The 6CM5 and 6DQ6 have identical pin connections, so can be interchanged with little trouble.

This article on voltage regulators will perhaps help some to get away from the feeling that banks of VR tubes are necessary to handle large voltages and currents. Both supplies work quite well although I feel currents in excess of 200 mA. may cause poor regulation at high output voltages with the large supply and no higher than 75 mA. in the case of the smaller, although 60 mA. may be a safer figure for best regulation.

A variant of the smaller supply is used quite a bit in some Yaesu Musen equipment. The larger supply is an adaptation of a supply published in Radiotron Designers Handbook.

One very desirable feature of these types of supplies is that you are not tied to a definite regulated output voltage as by just varying the position of the slider on the voltage control potentiometer, a reasonable range of output voltage can be obtained.

AUSTRALIAN RADIO AMATEUR

CALL BOOK

1969-70 EDITION

NOW AVAILABLE



Get your copy now from your

Division or usual Supplier



Price 75c

W.I.A. D.X.C.C.

Listed below are the highest twelve members in each section. Position in the list is determined by the first number shown. The first number represents the participant's total countries less any credits given for deleted countries. The second number shown represents the total D.X.C.C. credits given, including deleted countries. Where totals are the same, listings will be alphabetical by call sign.

Credits for new members and those whose totals have been amended are also shown.

PHONE

VK5MS	318/346	VK5AB	297/314
VK8RU	313/338	VK4KS	297/302
VK3AH	311/326	VK4FJ	284/304
VK4HR	309/326	VK4TV	284/288
VK2JZ	306/324	VK2APK	271/283
VK6MK	303/323	VK3TL	271/277

New Members:

Cert. No.	Call	Total
102	VK2AXI	30/102
103	VK4SD	114/115
104	VK3LC	107/107

Note: Cert. No. 102 shown last month should read VK2AXI not VK4SD.

Amendments:

VK2AAK	270/275	VK4UC	199/199
VK2ZE	237/240	VK3AM	185/185
VK3ACD	232/235	VK3KF	155/155
VK4PX	216/217	VK3SX	145/148
VK4MY	202/202	VK4SD	114/115

C.W.

VK3AHQ	301/315	VK3APK	274/282
VK3QL	300/323	VK3YJ	271/288
VK3CX	289/312	VK3XB	270/287
VK4FJ	289/314	VK3ARX	269/278
VK4HR	288/297	VK3SX	266/289
VK2AGH	282/286	VK3NC	263/286

Amendments:

VK3RJ	246/260	VK4RF	135/147
VK4MY	152/152	VK4PX	104/106

OPEN

VK6RU	314/329	VK6MK	304/324
VK4HR	313/338	VK2EO	302/305
VK3AGH	311/326	VK4FJ	297/322
VK3VN	308/325	VK3APK	294/305
VK4SD	306/321	VK3ARX	292/301
VK4TY	306/321	VK3SX	288/307

Amendments:

VK3NC	264/275	VK4MY	226/226
VK4UC	246/247	VK4RF	199/211
VK3ACD	232/236	VK3SX	154/157
VK4PX	232/237		

The W8NWU Teeter Totter Tuners*

JOHN J. SCHULTZ, W2EYJ1

THE original article on T networks mainly emphasised their low-loss possibilities and their application in matching relatively short antennas on the low frequency bands.

W8NWU found a much wider application possible for this handy network, including usage at v.h.f. frequencies where the components for other networks may become trickier to adjust. He also found various inexpensive sources for the components that could be used in a variety of the lower frequency versions of a T network.

THE BASIC TEETER TOTTER

Fig. 1 shows the basic T network which was named the Teeter Totter. If both the input and output impedances are the same, the value of both capacitors will be the same at resonance. When the output impedance is greater than the input impedance, the

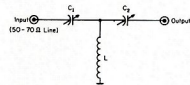


Fig. 1.—Basic Teeter Totter version of a T network.

value of the capacitor in the output leg will decrease to match the higher impedance at the output while the value of the capacitor in the input leg must increase in order to keep the combination of the two capacitors and the coil in resonance. When the output impedance is lower than the input impedance, the opposite setting of relative capacitor values is necessary. This seesaw action of the capacitor values resulted in the Teeter Totter name.

The circuit was tried on 80 through 2 metres. The range of impedances that can be matched depends upon the tuning range of the components used, but it will cover at least 4 to 1. That is, with a 50 ohm input reactive impedances from at least 12 to 200 ohms can be accommodated.

A typical circuit for use on 80 metres was constructed using a 20 μ H. coil and two 140 pF. variable capacitors. The

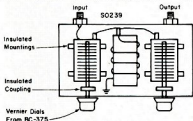


Fig. 2.—Construction of the network of Fig. 1 for 80 metres. Both capacitors are 140 pF. units from a BC375 tuning unit. The inductor can be a 20 μ H. unit, air wound from 1/8 inch copper tubing or wound on the ceramic form in the BC375 tuning unit, double spacing all but four turns at one end of the ribbed form.

* Reprinted from "CQ," February, 1969.

● The author's article on T Networks in the "CQ" issue of May, 1968, resulted in correspondence with various Amateurs who developed T Network designs. One of the most interesting variations on the theme of T Networks was W8NWU's series of tuners.

unit was constructed in a small aluminum enclosure using the components that were available from a surplus BC375 tuning unit. Although no power tests were tried, it would seem that the spacing of these capacitors and the heavy coil would allow operation with even a kw. rig. Fig. 2 shows the construction used.

CIRCUIT VARIATIONS

In order to eliminate the need for having to insulate the two variable capacitors from ground, the circuit of Fig. 3 was developed. Basically it works the same as the circuit of Fig. 1 except that it is a half-wave instead of a quarter-wave circuit. The proportionate amount of inductance in each leg varies according to the impedance ratio being matched while the impedance at the point where the variable capacitor is connected remains infinite. The range of impedances which can be matched is again at least 4:1.

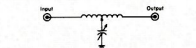


Fig. 3.—A variation of the basic network which allows use of a capacitor with a grounded rotor.

A simple procedure is possible to initially determine the coil and capacitor values. Both ends of the coil instead of being connected to any external circuit are grounded, each through a 50 ohm resistor (for use in a 50 ohm co-axial line at the input). The capacitor is placed at the centre of the coil. Then a grid dip oscillator is loosely coupled to the coil and tuned to the band of interest. The coil is symmetrically dimensioned and the capacitor value adjusted for resonance. The resistor representing the output load can be replaced by different values and the resistive range which the circuit can match determined as the components are resonated again for each different load value.¹

Fig. 4 shows the construction of such a tuner for use on 80 metres. The contact on the roller inductor must be modified to permit a separate lead to the variable capacitor. By removing the two t.v. doorknob capacitors, which are in series, from their parallel connection to the variable capacitor, the same component values will work on 40 mx.

Low power versions of the circuit, particularly for use on 10 metres, have

¹ You may use a low power exciter and s.w.r. meter to the network's input.

been constructed using XR-50 coil forms and 25-50 pF. receiver type variable capacitors. Such a circuit constructed in a minibox would be particularly useful, for example, at the base of a fixed station or mobile vertical antenna which didn't present an exact match to the type of co-axial line that was available. When the impedance transformation was not too great, as it would be when going from a 30-36 ohm whip base impedance to a 52 or 70 ohm co-axial line, no re-tuning of the circuit is necessary over any major segment of a band. Instead of a variable capacitor being used, the slugs in the coil form could also be used for tuning and a fixed 47 pF. mica capacitor used.

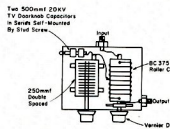


Fig. 4.—Construction of network of Fig. 3 for 80 or 40 metres utilising mainly BC375 components.

MULTIBAND VERSIONS

Multiband versions of either form of the network can be constructed as shown in Figs. 5(A) and 5(B). Which circuit is best is a moot question and the choice must be left to the individual builder. Each circuit has various constructional advantages and disadvantages. The circuit of Fig. 5(A) requires two insulated capacitor mountings but the dissipative losses in the capacitors may be less than in the inductors of Fig. 5(B). The arm of the inductor bandswitch can be grounded thus lowering its insulation requirements. The single capacitor of Fig. 5(B) is certainly easier to mount on a chassis. However, the insulation requirements of the inductor bandswitch, if it is mounted on a metal panel, may be rather high when a high impedance is being matched at the output.

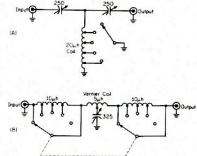


Fig. 5.—Two methods for constructing bandswitchable couplers. Typical values are shown which should allow complete 30-10 metre coverage. Coil taps must be found by experimentation for each band.

AUSTRALIS OSCAR 5 PROGRESS REPORT

RICHARD TONKIN*

The launching into orbit of the **Australis Oscar 5** satellite has been delayed by problems with the launch vehicle with which it is hoped the satellite will hitch a ride into space. However, it seems likely that the launch will occur before the end of the year. Latest launch information may be obtained by listening to the weekly W.I.A. Divisional broadcasts.

AMSAT have now completed the pre-launch tests on the satellite, which have been under way since May. The satellite has passed the rigorous vibration and thermal vacuum tests very successfully and it is now considered ready for launch.

A problem which arose in the command receiver ("A.R." November 1969, page 19) has now been at least partially corrected and it seems likely that the 29.450 Mc. transmitter will be switched on at about 0700 GMT each Friday and off at around 0700 GMT each Monday. This, of course, will conserve the satellite's chemical batteries and will enable both transmitters to operate for a longer period.

Final alignment of the satellite's transmitters resulted in the following power outputs:

29.450 Mc. transmitter 180 mW.

144.050 Mc. transmitter 120 mW.

These power outputs will gradually decrease as the battery runs down. It is expected that the 2 metre transmitter will operate for about six weeks and the 10 metre transmitter for more than eight weeks (at week-ends only).


Amateurs and S.W.'s intending to track the satellite should read the following articles which have appeared in "A.R.":

Australis Oscar "A"—Users' Guide,
February 1968, page 3.


Australis Oscar "A"—Users' Guide,
Part Two, March 1968, page 10.

Australis Oscar 5 Satellite Ready
for Launch, Oct. 1969, page 7.

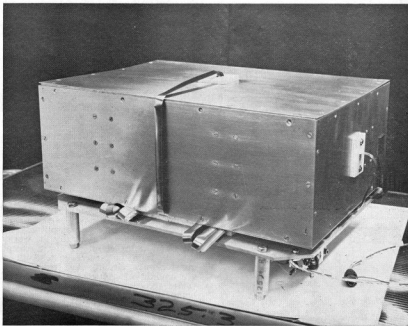The telemetry calibration graphs which appeared in the October 1969 issue of "A.R." are the ones which should be used by those tracking the satellite. Additional copies of the calibration graphs, telemetry reporting forms and information on when to listen for the satellite may be obtained from the Oscar State Co-ordinators, whose names appeared on page 7 of October 1969 "A.R."



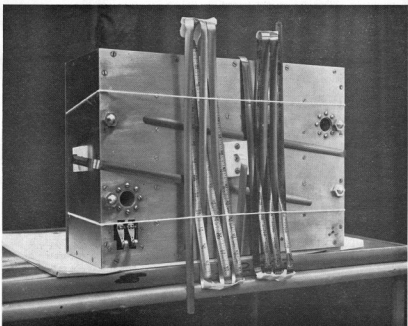The Australis Oscar 5 Satellite in launch configuration.



Antenna folding pattern.

* Chairman, Project Australis, 5/39 Tooronga Road, East Malvern, Vic., 3146.

OBSERVATIONS FROM AUSTRALIS OSCAR 5*

JAN A. KING, K8VTR

While tracking a satellite is an important and interesting Amateur activity, it is far from being the main objective of **Australis Oscar 5**. This is a telemetry satellite and reports information about itself as well as its environment; the former is useful to designers of future satellites and the latter gives data for ionospheric propagation and space research. Project **Australis-Oscar** and **AMSAT** need this information from every Amateur listening to the satellite. Some suggestions for observations are given below:

1. **Acquiring the satellite.**—Generally, listen for the 2 metre beacon before trying the 10 metre beacon, which may be on intermittently or only during week-ends. Observe telemetry channel 1 to see if the 10 metre beacon is on; a current of 50 to 60 mA. (during the first month of operation) indicates the beacon is on, while 25 to 30 mA. shows it is off.

2. **Temperature record.**—Keep an accurate record of the temperature (channels 5 and 7) during each part of a pass. Overhead passes will occur at your location around 1500 local time every day. Data for these and other passes is of interest for the thermal designer of future satellites. Of great interest is the temperature during the North-South pass at 0300 local time daily, when the satellite will be going through a dark (colder) period. Another useful measurement is the difference in temperature between the skin and inside of the space craft.

3. **Horizon sensor.**—This experiment is a first for Amateur Radio. Three horizon sensors are mounted on the satellite with the following alignment:

X axis sensor—parallel with the 2 metre antennas.

Y axis sensor—perpendicular to all antennas.


Z axis sensor—parallel with the 10 metre antennas.

When a sensor is not viewing the earth, the telemetry channel emits a tone between 510 and 640 cycles; when it views a portion of the earth, the tone will be higher, probably around 1000 to 1200 cycles. Measure these values for each axis and add them to your telemetry report.


A word of caution. If the satellite spin rate is high about a given axis, one or two sensors may have an on time shorter than the duration of the sampling period. In this case, be careful not to confuse the on-off transition with a telemetry channel change. Probably the spin rate around the Z axis will be slow (about 4 r.p.m.), but confusion may sometimes arise even at this slow rate.

Occasionally a short transition may occur on one of the sensors as it sweeps across the sun or the moon. Note the

(Continued on Page 24)

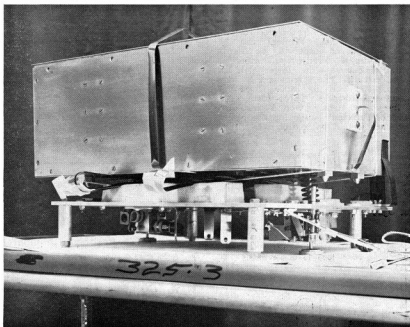

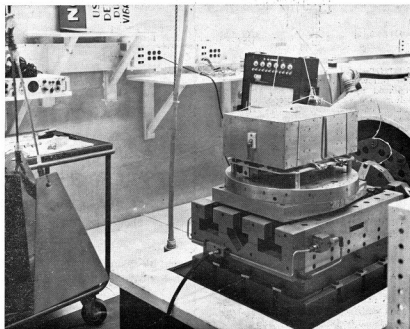Satellite on separation plate. Note separation spring.




Vibration test configuration.

Photographs by courtesy of National Aeronautics and Space Administration

* Reprinted from "AMSAT Newsletter," October 1969.

More on the Single-Loop, Triband Cubical Quad Beam Element

Experiments have shown that the energy transfer from the feedline to the radiator quad element can be greatly improved—especially on 10 mx—if a simple ferrite transformer is installed between the lower pair of tuned circuits. The ferrite is a 2" long 1/2" diameter rod, like those used for balun transformers. Three turns each bifilar and tightly wound insulated wire of sufficient gauge for the power used are wound on to the rod.

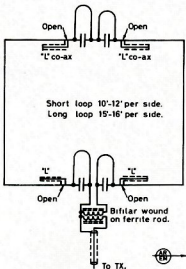

DJ2UT used with excellent results the following version: The coils are replaced by wire loops and the capacitors are formed by pieces of open ended co-axial cable. The radiator loop has 15 feet and the reflector 16 feet per side, this larger loop gives of course more gain and less "L" is needed for the tuning coils or loops. With the larger loop it was necessary to have a similar set of tuned circuits at the bottom and at the top of each quad loop, to prevent the radiation lobe on 10 metres from showing to one side.

The same tuning units were also used by him with a small loop, by extending it with four pieces of co-ax. (the far end short-circuited) instead of loading coils near the tuning units.

JA1BHG described in the JA Amateur magazine the translation of my "A.R." paper and his successful experiments with several forms of the single loop quad. Dimensions and s.w.r. graphs were published. Sorry, I can't read the JA text.

—H. F. Ruckert, VK2AOU.

PROVISIONAL SUNSPOT NUMBERS

AUGUST 1969

Dependent on observations at Zurich Observatory and its stations in Locarno and Arosa.

Day	R	Day	R
1	175	16	46
2	182	17	38
3	161	18	32
4	174	19	29
5	158	20	23
6	134	21	38
7	128	22	46
8	96	23	62
9	105	24	66
10	90	25	75
11	73	26	90
12	60	27	98
13	47	28	107
14	50	29	124
15	62	30	138
		31	114

Mean equals 90.9

Mean for February 1969: 107.6

Predictions of the Smoothed Monthly

Sunspot Numbers

November 93 January 90

December 92 February 89

—Swiss Federal Observatory, Zurich.

PROVISIONAL SUNSPOT NUMBERS

SEPTEMBER 1969

Dependent on observations at Zurich Observatory and its stations in Locarno and Arosa.

Day	R	Day	R
1	81	16	107
2	76	17	110
3	72	18	110
4	67	19	69
5	62	20	49
6	69	21	63
7	63	22	85
8	68	23	85
9	40	24	88
10	45	25	112
11	64	26	115
12	67	27	123
13	82	28	110
14	75	29	88
15	105	30	81

Mean equals 81.0

Smoothed Mean for March 1969: 105.3

Predictions of the Smoothed Monthly

Sunspot Numbers

December 87 February 84

January 85 March 82

—Swiss Federal Observatory, Zurich.

WIRELESS INSTITUTE OF AUSTRALIA FEDERAL EXECUTIVE

The Institute can now offer annual subscriptions to following Amateur Journals:

- ★ "QST"—Associate membership and renewals, \$6.40.
- ★ R.S.G.B. "Radio Communication" (ex "The Bulletin") is only sent with membership of Society. \$5.50. Send for application form.
- ★ "CQ" Magazine, \$5.70; Three Years, \$13.50.
- ★ "73" Magazine, \$5.50; Three Years, \$11.50.
- ★ "Ham" Magazine, \$5.50; Three Years, \$11.50.

R.S.G.B., A.R.R.L., "CQ" and "73" Publications available.

Send remittance to Federal Executive, C/o. P.O. Box 36,
East Melbourne, Vic., 3002.

Receipt of your first issue will serve as acknowledgment of your sub. Allow six weeks for delivery.

FOR A BETTER DEAL

When purchasing SWAN EQUIPMENT be sure to purchase from the
SWAN FACTORY Authorised Distributor for Australia—

W.F.S. ELECTRONIC SUPPLY CO.

12 Bowden Street, North Parramatta, N.S.W., 2151,
Phone 630-1621, or Swan Electronic Service Co.,

14 Glebe Street, Edgecliff, N.S.W., 2027,

and be assured of an honest deal backed up by the integrity of the
huge SWAN ORGANISATION, and full factory warranty, service
and spare parts.

Ask for details of our hire purchase facilities.

We accept trade-ins on all equipment.

Good used equipment available.

Transistors on Computer Boards—Some Further Thoughts

R. L. GUNTHER,* VK7RG

IN Part 1 of this series ("A.R." Aug. 1969) were described the approximate electrical characteristics of the transistors which have been found on computer circuit boards. It is possible that other types will be discovered, but those were the only ones we saw, out of many thousands examined. In the following discussion, I shall investigate related topics in somewhat more detail.

ILLEGIBLE NUMBERS

From time to time the number designation has been rubbed off the top of a transistor. There are several ways to meet this problem.

(1) Compare the board with others. If an identical configuration of parts is found, numbers may be read from the other board.

(2) Do a few simple tests: PNP/NPN, BV_{CEO} v. BV_{CBO} , BV_{EBO} . That will tell you the polarity, whether the transistor is alloy junction (e.g. 033, 083) or alloy diffused (e.g. 015, 065), and whether it is likely low power (e.g. 033) or medium power (e.g. 030).

(3) At the worst, if you don't know the number, it won't matter in most instances, as long as you know the polarity. Most transistors are 033, 083, or similar, and you are not likely to be wrong if you make that assumption. If application is other than that of "general purpose" type, tests could be useful, depending on specific characteristics required. For properties such as low noise or high voltage or high gain, individual testing is necessary in any event.

BREAKDOWN VOLTAGES

There is no need to panic when you see apparently obscure designations like " BV_{CEO} " and related parameters; this is the shorthand of transistor voltage designations, and as we discussed in Part 1, they can be very useful to untangle the voltage rating behaviour of a transistor under various conditions. The main points to be made are these: If resistance in the base circuit is relatively high (e.g. over a few kilohms for ordinary types), the collector breakdown voltage drops sharply, finally ending at BV_{CEO} with infinite base circuit resistance. Unfortunately, there is so much variation in BV_{CBO} between individual transistors, there is no way to forecast this behaviour except by testing each unit, if voltage rating matters.

Another point is that voltage rating may matter more often than you believe. If there is an inductive load, collector voltage can rise to alarming levels, particularly if the collector current is pulsed, e.g. in Class C, or even in Class A if the transistor is overdriven on a peak. A peak, that is all it needs if you are too close to BV_{CBO} . Take note.

The other point where voltage matters is the problem of overdriving amplifiers in Class C; I have discussed this at length in the series on transistor transmitter design in late 1967 issues of "E.E.B." and in "Amateur Radio" (Sept. 1967, p. 14), and there is no need to go into it further here. But bear in mind that you cannot, without impunity, crank up the drive on a transistor as you would a valve, particularly if the base is already back-biased (even by a base-leak). If you don't believe this, try it on an 015 or 065 with various values of drive and bias; this can be illuminating, and it can also give you a feel of the limits to which you can push these transistors. It is practical in this instance because of the unusually low cost of these items.

These germanium transistors can resist transients somewhat better than silicon, because of their relatively sloppy reverse characteristics, but there is more latitude among the TO-5 case types than in the TO-18 (small) case ones. Owing to their low leakage and high impedance characteristics, the TO-18 types are often as sensitive to overvoltages as silicon; I have punctured them with as little as 3 μ A. of reverse current, collector to base. They are best tested by constant-current methods, as described in "E.E.B." for May 1967.

Perhaps you may be interested to know why the BV_{EBO} characteristics of the alloy junction (e.g. 033) types differ so much from all the others. It is caused by the symmetrical arrangement of the collector and emitter dots on the base chip; this causes about the same breakdown level on either side:



The other types all have better frequency response and a much lower base-emitter than collector-base breakdown. This will also be evident from the construction of the diffused alloy types:



This geometry reduces transit times, depletion layers, etc., and improves frequency response greatly. The mesa types are similar, but with part of the collector chip etched away. Planar add further degrees of sophistication; I must write an article about this one day for "A.R." or "E.E.B."

There is a peculiar property transistors show when there is a very high resistance in the base circuit. As collector-emitter voltage increases, the collector current will increase sharply at BV_{CEO} , as one would expect, but it

rises faster than it ought. If the power supply is current limited (as with a large resistor), the collector voltage will be seen to increase and whereas collector current increases, the collector voltage will decrease. If you continue to increase I_{CB} , second-breakdown will occur, and the junction will vanish. But between these two points, the collector shows a negative resistance characteristic. It seems reasonable to assume that this occurs because, with no external current possible to the base, leakage from the collector forward biases the base, increasing collector current, thereby lowering collector voltage. This property has been put to practical use with computer transistors for an oscillator in a signal injector circuit,¹ and many applications suggest themselves. A similar effect (though for different reasons) can be observed just beyond the zener point of some diodes, allowing them to be used as oscillators! This may be verified quite simply while testing reverse characteristics of a batch of diodes, if you place a small transistor radio near the testing power supply. As you pass the zener voltage, some diodes will cause a noticeable series of squawks or buzzes at r.f., presumably from a kind of tunnel-diode action in combination with distributed inductance and capacitance of the power supply circuit.

On a more serious level, the whole phenomenon of second breakdown is well covered in the "R.C.A. Silicon Power Circuits Manual," beginning on p. 84.

EFFECT OF HEAT ON FREQUENCY RESPONSE AND BETA

Although some of us who were involved with testing these transistors are not wholly in agreement, it is possible that the spread of f_T actually found has been made large by adverse effect of heating while desoldering—through circuit abuse. This would have the effect of lowering the apparent minimum. Rather, I should say the actual minimum, since once the frequency response has been degraded, the change is permanent.

In any event, we have definite evidence that excessive heat can introduce instabilities, and lower punch-through voltage and impedance. If, then, you want to preserve optimum operating characteristics of the transistors, the minimum possible desoldering heat should be employed. Preferably, high frequency transistors should be removed from boards by sawing them out, leaving some of the printed circuit wiring attached for easy connection. If sufficient board is included with the transistor, it can also provide a simple means of supporting or mounting it.

Beware, therefore, of claims that "circuit board transistors can stand a lot of heat." They can, but may suffer in some respects even though they still

1—"E.E.B." June-July 1967.

* 23 Waterworks Road, Dymyrrne, Tas., 7005.

amplify. Indeed, a strange result is that they may amplify even better! (at low frequencies). I performed a number of tests in which transistors were forced to dissipate about 5 watts for several seconds. The result was that the alloy diffused types increased their d.c. amplification factor (β) from 10% to 50%, but the alloy junction types were apparently unaffected. An increase of β , so obtained, was permanent, but slightly too much heating could degrade it suddenly. Presumably the heating decreased the frequency response while increasing the d.c. amplification factor. Amazing!

ACTUAL HIGH FREQUENCY PERFORMANCE


The figures given in the Tables of Part 1 of this series were mostly obtained (by an engineer friend) from actual measurements of f_r , by measuring the slope of f_{osc} with f above f_{osc} . It seemed to me, however, that a practical way to evaluate the high frequency performance of a transistor would be to use it in an actual circuit. The simplest way to do this is to make the transistor part of a feedback oscillator. The maximum frequency of oscillation may be taken as a guide to the upper limit of performance of a given transistor. It may amplify up to that frequency, but it certainly won't amplify much beyond it under ordinary experimenters' conditions, because the transistor oscillates in the first instance only because it still amplifies. You can assume that an ordinary Hartley or Colpitts configuration will give the maximum practical amplification/oscillation frequency for a given transistor connected in common-emitter configuration. The maximum practical frequency for a transistor in common-base is suggested by the maximum oscillation frequency of a common-base oscillator,² assuming good geometry for both. I take the liberty of reproducing here (Fig. 1) a circuit which has been used (for this purpose). When C_1 is large (e.g. 100 pF.), the oscillator behaves like a tapped-coil type. When C_1 is minimum, the oscillator is essentially parasitic, or common-base type with feedback only via the internal capacities of the transistor. Further details of theory and use may be read in the "Break-in" article, which, incidentally, will be re-printed in "E.E.B."

I have called the maximum oscillation frequency so obtained, " f_{osc} ". It is not necessarily equivalent to f_{osc} ; the latter is the maximum theoretical frequency at which a transistor will amplify, i.e. when power gain is unity. Because of the usual circuit inefficiencies, P.G. was much likely higher than that for maximum frequency of oscillation here. I did, however, find an apparent relationship between f_{osc} and f_r , as shown in this chart:

Type	f_r^* Mc.	f_{osc}^* Mc.	F [†]
Mesa	100-300	25-100	25-40
Alloy diffused	40-100	25-45	25-50
Alloy junction	~4-20	5-20	80-150

(* At 5V./2mA.)

Here, $F = f_{osc}/f_r$. If F were constant, this relation might allow you to find f_{osc} or f_r if one were known. f_r will be constant for a given type of transistor, within the production limits. But f_{osc} depends not only on f_r , but also on base resistance and collector capacitance. Since each of these can vary widely from one transistor to another, our engineer friend maintains that there is no great value in finding values for F . In addition, he points out that f_{osc} will also depend on the matching of the oscillator to the input and output impedance of each transistor.

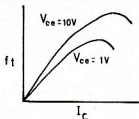

Effect of collector voltage and current on f_t .

Although this is true, I maintain that there is a consistent pattern of F for a given transistor type, as shown in the above chart, and that f_{osc} is a useful parameter because of its obvious practical value.


From the chart it may be seen that F is about the same for the first two types, but that f_{osc} is about the same as f_r for the low-frequency ones. This has practical value, because it shows that appreciable performance can be obtained even from the "low frequency" types (compare with OCT11), and that the oscillator performance of the high-frequency transistors is not as impressive as the range of f_r appears to indicate. Indeed, the TO-18s appear to be only slightly better than the TO-5s at $I_c = 2$ mA., even though the f_r of the latter is considerably higher. It is quite possible that this was caused by inadequacy of design of my test oscillator, but again this is the actual, not the ideal situation, therefore useful for you.

On the other hand, it is essential to realise that frequency response of a transistor depends on collector voltage and collector current. This may be seen readily by observing the gain-bandwidth product curves of various transistors. Owing to the varicap pro-

perties of the junctions, f_r increases with voltage, and increases to a maximum with current. The latter behaviour is well illustrated by the curves of Fig. 2 of the preceding article; f_r of a given type 153 went up from 270 Mc. at 1 mA. to 500 Mc. at 5 mA., and likely even higher at 10 mA.; for that same transistor f_{osc} was 240 Mc., just about the limit of my absorption wavemeter (used to measure the frequency of the test oscillator).

Since the average power dissipation limits of the TO-18 mesa types must not be exceeded, it is evident that their best response will be obtained under pulsed operating conditions (10-30 mA.), not surprisingly the condition found in computers. It would also apply to Class C, but most of the TO-18 types have too low a voltage rating for effective use in transmitter stages. They will work well indeed in receiver and instrument applications, and best with moderately high currents, as long as they do not become too hot. But they are best in their use as switches.

Conversely, because of the relatively constant f_r (with I_c) of the TO-5 alloy diffused types (015, etc.), they are not suitable for high speed switching in computers, because they saturate at low currents (e.g. 20 mA.), although they make good high frequency amplifiers. The alloy junction types (e.g. 033) do not saturate until currents of 100 mA. or so are reached, but their transient-response time is not good enough for use in switching circuits; they make lovely amplifiers, though. Unfortunately, data books do not always stress this difference between switching and amplifier behaviour, and even professional engineers can make the wrong choice (or so I am told by a professional engineer).

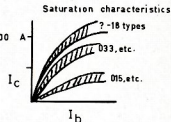

In summary, f_{osc} will often be a better guide to actual performance of transistors in a real circuit, than will f_r , though one must remember that it does depend on V_c and I_c , and that amplifiers may oscillate better than they will amplify at some high frequency—a fact which is well known to all students of Murphy's Law.³ The performance of the amplifier will also be highly dependent on geometry, neutralisation, and unilateralisation. This matter has been discussed in 1967 issues of "E.E.B." and will be the subject of a forthcoming article in "A.R." Under optimum conditions, a rule of thumb would say that the maximum useful common-emitter frequency (e.g. P.G. = 10 db.) will be found at quarter to half f_r , depending. But this is only useful if you know f_r .

3—If something can go wrong, it will!

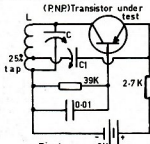


Fig. 1

Fig. 1.—Transistor frequency testing oscillator. L/C should be high for best response. C_1 : See text.

2—"The Common-Base Oscillator, and its Applications," by C. F. Smith, VK3CD, and R. L. Gunther, VK3RG, "Break-In", March 1968, p. 45.

SPREAD OF CHARACTERISTICS

Our engineer friend suggests that one reason for the wide variation found within a given type may be that some of the transistors developed faults during use, which made them unsuitable for computer use. After all, that is likely one of the reasons why the boards have been declared surplus in the first instance. It is possible that "typical" values lie above the pessimistic minima we have shown, and the results of our averages imply this. But again, the fact remains that these minima are the real values encountered by the experimenter stripping the boards. A transistor which may be degraded⁴ for computer use may be perfectly satisfactory for an experimenter, for many applications—as long as he is not building a computer!

In any event, the wide spread of characteristics within a given type makes nonsense of any attempt to specify commercial equivalent types. There is a superficial resemblance between the alloy junction types and the 2N1302-9 series; and alloy diffused types and 2N1300-1, 2N1654 or 2N1683; and the mesa types to 2N705, 2N711, 2N791 or 2N1204. The situation, however, of the connection of collector or base to case, and the fact that it is difficult to find adequate agreement with an average of important parameters, leads us to believe that these are special computer transistors manufactured specially for the purpose.

Since there is often more variation of characteristics with a given type number than between type numbers, and since these transistors appear to be special types, there seems little point in trying to find a specific type number that they can replace. The only sane procedure is to ascertain the principal characteristics of a transistor in a given circuit, and then choose computer board transistors which match it most closely. Those characteristics may be found from the various data manuals, or simply by circuit inspection; in an ordinary low power audio amplifier, virtually any of the transistors will work, having the correct polarity. In a circuit amplifying 1 Mc., the alloy junction types will suffice; for 10 Mc., the alloy diffused types; for 100 Mc. at low voltage, the small mesa types; above that use commercial transistors.

Even the difference between silicon and germanium is not always large. It may alter the bias requirements a bit, but this is easily done. In base-stabilised circuits, the germanium would need about one-quarter volt less base voltage than silicon. If the bias was not altered, the effect would be to increase the collector current of the germanium unit somewhat.

It is not really necessary to dwell on this matter of replacement, but I mention it only because I am constantly approached by desperate young men who must know "what shall I use to replace the transistor in this circuit; I can't buy it locally?" They look startled when I say that "it probably does not matter". In view of the fact that

in any handful of transistors you pick up, most of them will work in most circuits, it is truly depressing that manufacturers continue to issue their plethora of type numbers, each differing infinitesimally from the last.

TESTING TRANSISTORS

Throughout these pages we have insisted that the data charts can only be approximate guides to characteristics and that optimum use of a given transistor can only be obtained if you test it. If you test it, you will be able more effectively to design it into a circuit, by the simple rules of the excellent design articles which have appeared in "A.R." and elsewhere.

The extent of your tests will depend on your applications. For a simple LT AF oscillator you can probably take it as-is, without testing (though troubleshooting is facilitated if you know at least that you are starting with a good transistor). For critical h.f. work, a frequency test is desirable; use the oscillator of Fig. 1, and measure its maximum frequency with an absorption wavemeter (or with a g.d.o. if the test oscillator is just beyond the maximum frequency). For h.t. power supply or r.f. power amplifier work, a voltage test and possibly BV_{CE} test is indicated, particularly if there is appreciable resistance in the base circuit to be used. For a.f., a gain check can show you the best transistors to use when high gain is desirable in a stage (high gain isn't always necessary).

One important property of transistors is often overlooked when testing; the amplification factor (e.g. β) can vary appreciably with different values of collector current; the more linear is the characteristics, the less is this variation (viz., shallower slope, $d\beta/dI_C$). This behaviour is most clearly visualised by examining h_{FE} v. I_C curves from various data sheets, and in lesser degree, from the curves in Part 1 of this series. Therefore, it is better to test a transistor at the current at which it will actually be used, than at some arbitrary level (usually 1 mA.). The conventional 1 mA. figure may be all right for ordinary lower power types, but it tells you nothing about intermediate (2N1038 or 028) or high power (2N301, 036, 042, 2N1100) types. In addition, it may be useful to know the actual linearity of a transistor—as when choosing for units to go into a low-distortion amplifier.

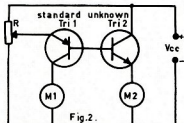


Fig. 2—Simple transistor gain tester (by L. J. Yelland). For low power transistors, R can be 5K, smaller for higher power; V_{CC} at least 6V., preferably same voltage as used for test transistor in actual application.

A very clever and useful device for making such tests simply has been suggested by L. J. Yelland, of Melbourne, to whom I am grateful for the circuit of Fig. 2. Tri 1 is a standard transistor whose gain is known as a function of collector current (a calibration curve as in Fig. 3 can be kept at hand). Tri 2 is the transistor under test. Note that the two transistors must be opposite polarity, but same type (e.g., germanium, same power range, etc.). Where I_1 is the current read on M_1 , and I_2 on M_2 , R is adjusted until I_1 is at the desired level, whence

$$h_{FE2} = (I_2 \div I_1) (h_{FE1})$$

or

$$h_{FE2} = I_2 (h_{FE1} \div I_1).$$

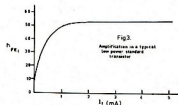


Fig. 3.

This avoids the nuisance of having to measure very small base currents, and measures gain at actual current levels desired, quickly. A calibration curve of gain v. current should be made for each standard transistor, e.g. Fig. 3. From this should be made a plot of $(h_{FE1} \div I_1)$ v. I_1 , as in Fig. 4 (merely an example, please note). From the right hand form of the above equation, it may be seen that the d.c. current gain of the unknown transistor (No. 2) can be obtained simply by multiplying I_1 by the fraction obtained from a Fig. 4-type plot. Indeed, for simple general tests, where I_1 is taken at a standard 1 mA., the gain of transistor 2 may be read directly from the ordinate.

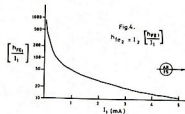


Fig. 4.

I should like to express my appreciation for the help and insights received from R. W. Brown, VK7ZRO, R. S. Maddever of Geelong, Vic., and our engineer friend who has been so patient and helpful.

CHANGE OF ADDRESS

W.I.A. members are requested to promptly notify any change of address to their Divisional Secretary—not direct to "Amateur Radio."

4—C.F. "E.E.B.", May and June 1967, Sept. 1968.

Burglary at VK2WI (Dural) and also at Crows Nest

The New South Wales Division's station at Dural was burgled some time on Thursday night, 23rd October. It would appear that the burglary was done by person or persons with an intimate knowledge of the station and its equipment.

Set out below is a list of items stolen. If anyone knows anything at all regarding the present location of any of this equipment, or if anyone is offered any of the equipment, they are requested to contact Gordon Clarke, Divisional President, by Phoning 94-2353 (work) or 94-6596 (home).

Any information will be handled with the strictest confidence.

- 1-Pye 20 watt a.m. v.h.f. Transmitter Type P.T.C. 330N, Reference No. 2844G, Serial No. 113. With Type D Crystal for 53.886 Mc.
- 1-Pye a.m. v.h.f. Receiver Type P.T.C. 3022N, Reference No. 2844S, Serial No. 136, with Type D Crystal for 53.886 Mc.
- 1-Kingsley Type AR7 Communications Receiver, Serial No. 1171, Chassis No. 02025, with "D" band coil box and 3 metre converter.
- 1-Kingsley Type AR7 Communications Receiver, Serial No. 246B/S1746, Chassis No. 01407, with "D" band coil box and 30 metre converter.
- 5-Coil boxes for Kingsley Receivers.
- 3-Power Supplies for Kingsley Receivers, 250 volt a.c., 12v. d.c.
- 1-825B transmitting valve.
- 2-Quartz Crystals Type D, frequencies 2247.916 Kc. and 11190.0 Kc.
- 2-Quartz Crystals Type 5587 holders, frequency 3325 Kc.
- 2-Quartz Crystals Type 5587 holders, frequency 3573 Kc.
- 1-Beat Frequency Meter, Type BC221.
- 1-S.W.R. Meter, "2WI" stencilled on case.
- 1-Philips Cathode Ray Oscilloscope, "2WI" stencilled on case.
- 1-A.W.A. Portable Beat Frequency Oscillator, "2WI" stencilled on case, Type 4R7490, No. 786.
- 5-Co-ax. Cable Connectors, Type PL259.
- 1-Desk Microphone and Control Box with pilot light and push button.
- 1-Palco Valve Testing Set.
- 1-Multimeter.
- 2-Pairs Headphones with plugs and cords.

The N.S.W. Division suffered another blow on 12th November, 1969, when the offices at 14 Aitchison Street, Crows Nest, were broken into and the following equipment stolen:

- 1-Hallcraft Communications Receiver, Model SX111, Serial No. 1110109/23166.
- 1-R.C.A. Communications Receiver, Type AR68. No serial number.
- 1-Paros Transceiver.
- 1-only 522 transmitter, no serial number. Mounted on 19 x 9 inch blue metal panel.
- 1-only 522 Transmitter and Receiver in black case.
- 1-Adcola Soldering Iron, 240 volt.
- 1-A.W.A. Type MR10B Carphone with 240v. a.c. power supply.
- 155-2N3819 Semiconductors.
- 8-V.h.f. Pre-amps.
- 2-Six Metre Converters.
- 75-T1588s.
- 150-TT3564s.
- 40-2N3055s.
- 50-NJ480s.
- 7500-Resistors.
- Call Books, Log Books, P.M.G. Handbooks, and coil formers.

AUSTRALIS OSCAR 5

(Continued from Page 19)

time, particular sensor, and tone frequency when this happens. Also note if the signal is in a null or a peak at the time. You may like to compute the exact attitude of the space craft and to correlate it with the signal strength and polarisation of the two beacons.

The X axis sensor data can be used to assess the effect of the magnetic attitude stabilisation system; the X axis spin rate should gradually decrease during several days as the axis comes into alignment with the geomagnetic field.

4. The propagation experiment.—The 10 metre beacon operating at 29.450 Mc. is potentially *Australis Oscar 5's* most important source for scientific information. It also requires greater sophistication on the part of the Amateur.

To fully participate it will be necessary to track both beacons simultaneously and preferably to record them on magnetic tape or paper charts.

Estimate the time when you expect to acquire the satellite and start listening several minutes beforehand. Note the time difference between acquisition of the two signals (2 metre and 10 metre). Similarly, note the time difference between loss of signals. Note any anomalies.

Using the 2 metre signal as a reference, try to time correlate the 10 metre signal to it. Make corrections for any pointing errors with either antenna. Discount the fairly regular nulls in signals caused by satellite spin.

An interesting number to be reported would be S_{10}/S_2 , i.e. the ratio of signal strengths at 10 metres and 2 metres, measured in linear units or in db. Compute this ratio for as many points during a pass as possible. Compare it with similar passes on other days. Does it stay particularly large or small during certain periods? Check for other Amateur activity at 10 metres affecting the observed signal.

The S_{10}/S_2 observations assist in the analysis of ionospheric effects at the two wavelengths. In addition, try to observe antipodal reception by listening for the 10 metre signal when the satellite is on the exact opposite side of the earth from you. Such observations should be well documented and reported to Project *Australis*.

5. Other experiments.—The above list is not comprehensive. Imaginative Amateurs will certainly think up many new experiments. If you have any ideas or suggestions, please send them in. Remember, your participation is essential to the continuation of an Amateur satellite programme.

THE F.M. SYSTEM

(Continued from Page 9)

tion, it has further been brought to light that the greatest irritating noise generated is located from 3 Kc. up. To reduce the effect of this noise, a pre-emphasis network is inserted in the audio section of the transmitter. Its purpose is to boost the frequencies above 1 Kc.

At the receiver there is a de-emphasis network to reduce frequencies above 1 Kc. to their original values. The overall effect is a return of the signal to its proper relative proportions, but with a considerable reduction in noise.

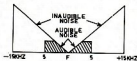


FIG.11.

Fig. 11.—Improvement in noise reduction due to pre-emphasis circuit in transmitter.

Another beneficial effect of de-emphasis is concerned with the noise produced by another signal or the ever-present random noise.

As previously noted, the greater the difference between the carrier frequency and the interference, the greater the indirect f.m. produced. By the use of the de-emphasis network, the triangular response of Fig. 10 is modified to the trapezium of Fig. 11. The de-emphasis action, by reducing the level of all frequencies above 1 Kc., slices off a considerable portion of the noise.

I trust that this article has been able to shed some light on the rather neglected subject of the theory behind the f.m. system and it will enable Amateurs to speak with a little more authority about the effects observed in their equipment.

INOUE IC-700

My quest, in Japan, was for modern high quality Amateur equipment of very good value. INOUE is selling in Japan, England, Germany, U.S.A. and elsewhere. The IC-700 Transceiver covers all Amateur bands from 3.5 to 29.7 Mc. in 500 Kc. segments with 1 Kc. read-out; plus WWV (10 Mc.). Using 9 Mc., 2.4 Kc. filters in both rx and tx, this single conversion design is free of unwanted spurious. Sensitivity is better than 1 μ V. for 10 db S+N/N ratio. Operates on a.m. or c.w. (500 c. bandwidth) and s.s.b.

BOOMLESS QUAD

Identical electrical spacing on 20, 15, 10. Centre Castings c/w. bolts \$10 pr. Canes 16-18 ft. \$1.25 ea. \$8 per set. Fibreglass 11.5 ft. long \$9 ea. Kits triband, complete (castings, canes, wire and nylon line) \$30. Prices include Sales Tax. Freight forward.

S. T. CLARK

26 Bellevue Av., Rosanna, Vic., 3084

Phone 45-3002



JOHN MOYLE MEMORIAL NATIONAL FIELD DAY CONTEST, 1970

SATURDAY, 7th FEBRUARY, TO SUNDAY, 8th FEBRUARY, 1970

The Federal Contest Committee of the Wireless Institute of Australia invites all Australian Amateurs and Short Wave Listeners to participate in this Annual Contest, which is held to perpetuate the memory of John Moyle, whose efforts advanced the Amateur Radio Service.

There are two divisions of this Contest, one of 24 hours continuous duration, and one of 6 hours continuous duration. The six-hour period has been included to encourage the operator who is unable to participate for the full 24-hour period. The 24-hour continuous operation is to be chosen by operator from 0600 GMT.

Operators using 25 watts or less input to the final stage will be considered for a certificate where his activity warrants its issue.

DATE

From 0600 GMT, 7th February, 1970, to 0800 GMT, 8th February, 1970.

OBJECTS

The operators of Portable and Mobile Stations within all VK Call Areas will endeavour to contact other Portable/Mobile and Fixed Stations in VK Call Areas and Foreign Call Areas.

RULES

1. There are two divisions, one of six (6) hours, and one of twenty-four (24) hours duration. The six-hour period for operating may be chosen from any time during the Contest, but the six-hour period so chosen must be continuous. In each division, there are six sections:—

- Portable/Mobile Transmitting, Phone.
- Portable/Mobile Transmitting, C.W.
- Portable/Mobile Transmitting, Open.
- Portable/Mobile Transmitting, Multiple Operation, open only.
- Fixed Transmitting Stations working Portable/Mobile Stations, open only.
- Reception of Portable/Mobile Stations.

2. All Australian Amateurs are encouraged to take part. Operators will be limited to their licensed power. This power shall be derived from a self-contained and fully portable source.

(a) Portable/Mobile Stations shall not be situated in any occupied dwelling or building. Portable/Mobile Stations may be moved from place to place during the Contest.

No apparatus shall be set up on the site earlier than 24 hours prior to the Contest.

All Amateur bands may be used, but no cross band operating is permitted. Cross mode operation is permitted.

Entrants in Section (d) for Multiple Operator Stations can set up separate transmitters to work on different bands

at the same time. All such units of a Multiple Operator Station must be located within an area that can be encompassed by a circle not greater than half a mile diameter.

For each transmitter of a Multiple Operator Station a separate log shall be kept with serial numbers starting from 001, and increasing by one for each successive contact. All logs of a Multiple Operator Station shall be submitted by the operator under whose Call Sign the transmitters are working. No two transmitters of a Multiple Operator Station are permitted to operate on the same band at any time.

3. Amateurs may enter for any section.

4. One contact per station for phone to phone, also one for c.w. to c.w. per band is permitted. Cross mode operation will be accepted for scoring.

5. Entrants must operate within the terms of their licences and in particular observe the regulations with regards to portable operation.

6. The exchange of serial numbers, consisting of RS or RST report plus three figures, commencing with 001 and increasing by one for each successive contact by the VK Station, shall be proof of contact.

7. Scoring—

(a) Portable/Mobile Stations:

For contacts with Portable/Mobile Stations outside entrant's Call Area 15 points

For contacts with Portable/Mobile Stations within entrant's Call Area 10 points

For contacts with Fixed Stations outside the entrant's Call Area 5 points

For contacts with Fixed Stations within the entrant's Call Area 2 points

(b) Fixed Stations:

For contacts with Portable/Mobile Stations outside entrant's Call Area 15 points

For contacts with Portable/Mobile Stations within entrant's Call Area 10 points

8. The following shall constitute Call Areas: VK1, VK2, VK3, VK4, VK5, VK6, VK7, VK8, VK9 and VK0.

9. All logs shall be set out under the following headings: Date/Time (G.M.T.), Band, Emission, Call Sign, RST/No., Sent, RST/No., Received, Points Claimed. Contacts must be listed in numerical order.

In addition, there shall be a front sheet showing the following information:—

Name.....Address.....
Call Sign.....Section.....
Division.....(6-hour or 24-hour)
Points Claimed.....
Call Sign of other op./s (if any).....
Location of Portable/Mobile Station.....
From.....hours to.....hours

A brief description of equipment used, and points claimed, followed by the declaration:

"I hereby certify that I have operated in accordance with the rules and spirit of the Contest."

Signed.....Date.....

10. The right is reserved to disqualify any entrant who, during the Contest, has not observed the Regulations and the Rules of this Contest, or who has consistently departed from the accepted code of operating ethics.

11. The decision of the Federal Contest Manager of the Wireless Institute of Australia is final and no disputes will be entered into.

12. Certificates will be awarded to the highest scorer of each section of each division. Additional certificates may be issued at the discretion of the F.C.C. The six-hour certificates cannot be won by a 24-hour entrant.

13. Return of Logs:

All entries must be postmarked not later than 28th February, 1970, and be clearly marked "John Moyle Memorial National Field Day Contest, 1970," and addressed to:—

Federal Contest Manager, W.I.A.,
Box N1062, G.P.O.,
Perth, W.A., 6001.

RECEIVING SECTION

14. This section is open to all Short Wave Listeners in VK Call Areas. The Rules shall be the same as for the Transmitting Stations, but may omit the serial numbers received.

Logs must show the Call Sign of the Portable/Mobile Station heard, the serial number sent by it, and the Call Sign of the Station being worked.

Scoring will be on the same basis as for Transmitting Stations. It will not be sufficient to log a station calling CQ. A portable/mobile station may be logged once only for phone and once only for c.w. in each band.

Awards: Certificates will be awarded for the Highest Scorer in each Call Area, for the 6-hour and the 24-hour divisions.

Example of Victorian S.w.'s Log

Date (Time GMT)	Band	Call Sign Heard	RST No. Sent	Station Worked	Points Claimed
7/2/70 0600 GMT	80 mx	VK2AAH/P	59001	VK3ATL/P	15
0610	80 mx	VK3ATL/P	59006	VK3GV	10
0620	40 mx	VK2AAH/P	59004	VK6VF/P	15
0640	20 mx	VK3GV	59015	VK3QX/P	*
0900	20 mx	VK4OF/P	59040	VK4OX/P	15

* No claim Fixed Station.

New Equipment

HY-GAIN LIGHTNING ARRESTOR




The precision-built Model LA-1 will safely by-pass to ground 10 or more direct lightning strokes. It is designed for installation in any standard 52 or 72 ohm co-axial feedline, and effectively removes static build-up around your antenna system, thus reducing the possibility of your equipment being hit by a direct stroke of lightning.

The unit will accept type SO-239 u.h.f. co-ax. connectors, the insertion loss is negligible, and weight is 5 oz. Price \$29 including sales tax.

Further information from Ball Electronic Services, 60 Shannon St., Box Hill, Vic., 3129.

SWE-CHECK FET METER

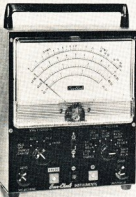

A new addition to the range of quality test equipment available from Radio Parts Pty. Ltd. is the Swe-Check "Volt-Ohm-A" FET Meter. Of robust, plastic coated, steel construction, the meter case has a 60° tilting device to enable easy readout when bench mounted.

Ranges—DC volts: 0-1, 3, 10, 30, 100, 300, 1K and 3K. AC volts: 0-3, 10, 30, 100, 300 and 1K. DC current: 0-300 uA., 1 mA., 10 mA., 100 mA. and 1 A. Ohms: R x 1 to R x 1 meg. in seven ranges. Price \$99 plus 15% sales tax where applicable.

Further details from Radio Parts Pty. Ltd., 562 Spencer St., Melbourne, or city and suburban branches.

Correspondence

Any opinion expressed under this heading is the individual opinion of the writer and does not necessarily coincide with that of the Publishers.

RADIO OPERATOR OF THE ILL-FATED "NOONGAH"

Editor "A.R.," Dear Sir,

It may not be realised by some of your readers that S. R. Pedemont, VK2BSP, who appeared in Silent Keys last month, was the Radio Operator of the "Noongah" lost at sea in August.

He was a "first tripper," and had just joined the ship in Port Kembla on what was to be her last voyage. Although suffering from severe sea-sickness, he cleared his distress traffic in a very efficient manner. Everyone who heard the distress messages agreed that the general operating procedure and "flap" of Mr. Pedemont was amazing, considering his lack of marine experience and the stresses he must have been under at the time.

I feel that his Amateur Radio experience must have contributed to the cool manner in which he discharged his duties on this tragic occasion, and that he deserves salutations from his brother Amateurs for a job well done.

—Noel Roberts, VK3NR.

C.W. REQUIREMENTS

Editor "A.R.," Dear Sir,

I am prompted by VK2ZFQ's letter in October "A.R." to make some comments concerning the c.w. requirement in the A.O.C.P. examination. I am convinced that the time has come to eliminate this archaic, unnecessary and unjust section of the examination. Further, I have very grave doubts as to the wisdom of introducing a Novice licence which included a c.w. requirement. My experience shows that the principal factor that is at present deterring a number of prospective Amateurs is, in fact, the c.w. examination. This fact is borne out by the great popularity of the Limited licence. Surely the main aim of the introduction of a Novice licence is to popularise Amateur Radio, and surely the saddling of the Novice licence with a c.w. examination would defeat this purpose.

The answer to the problem is, of course, to abolish the present c.w. requirement in the A.O.C.P. examination, without lowering the standard of the theory section. The standard of scientific education nowadays is so high that very few candidates have much trouble with the theory paper, but the c.w. test is a different kettle of fish!

However, I also base my opposition to the c.w. requirement on several other grounds, and these are as follows:—

(1) There are many Amateurs (like myself) who have found that they have neither the time nor the aptitude to master the art of c.w. Why should such Amateurs be denied the use of six of their bands simply because they are not proficient in c.w. And c.w. is such a necessary thing, why is it not made compulsory for the v.h.f. bands as well as for h.f.?

(2) There are many Amateurs (including full A.O.C.P. holders), whose main interest lies in phone operation, and who would seldom (if ever) want to pound the brass. Why should these Amateurs be required to pass an examination in a mode they do not intend to use?

(3) VK2ZFQ says that c.w. is the most effective mode for weak signal DX work, and that phone has its limitations for DX of that sort. This is very true; I quite agree that c.w. occupies a most important place in Amateur practice. However, I cannot agree that this is any justification at all for imposing a c.w. examination on all Amateurs. Many Amateurs may not be interested in weak signal DX work, and there are many like myself who still prefer the more personal touch of the microphone, even for DX work.

(4) I feel that it is unfair to stratify Amateurs into different classes such as "Full", "Limited", and so on. After all, we are all Amateurs, and all Amateurs should be permitted to operate on any and all Amateur bands, provided their technical knowledge and operating procedure are of a certain standard. The restrictions at present imposed on Limited licensees are contrary to their rights as licensed Amateurs.

Finally, let me reiterate that I am not opposed to c.w. as a mode, and am I opposed to the holding of c.w. examinations. Certainly, no one should be permitted to transmit c.w. unless they are capable of so doing, and an examination is the best way of making sure

of this. However, why should a pass in the c.w. examination be a prerequisite for phone operation on the DX bands? Let's be fair about this: certainly there must be a c.w. licence for those who want it, but why force it on those who don't? And why should those Amateurs who are not interested in c.w. be penalized by being deprived of the use of six of their bands?

I hope that these comments will arouse some discussion of the c.w. question amongst the readers of "A.R."

—John Martin, VK3ZJC.

☆

AUSTRALIA TO CORNWALL, U.K., WITH ONE WATT S.S.B.

G6KX, on holidays in Australia and using the call VK7LM/P VK2 worked G3DDN and G2ATQ on 21/10/69, frequency 14155, using a one-watt s.s.b. rig. Reports from both Cornwall stations to him were R5/S3. How's that for long path DX on QRP?

LOW DRIFT CRYSTALS

☆

1.6 Mc. to 10 Mc.,
0.005% Tolerance, \$5

☆

10 Mc. to 18 Mc.,
0.005% Tolerance, \$6

☆

Regrinds \$3

THESE PRICES ARE SUBJECT
TO SALES TAX

SPECIAL CRYSTALS: PRICES ON APPLICATION

MAXWELL HOWDEN

15 CLAREMONT CRES.,
CANTERBURY,
VIC., 3126
Phone 83-5090

Overseas Magazine Review

Compiled by Syd Clark, VK3ASC

"BREAK-IN"

September 1968—

Stand-by Battery Float Charger, ZL1BHN. How to keep your car or field day batteries fully charged. Should appeal to some v.h.f. operators.

A 9 Mc. Bilateral I.F. Amplifier, ZL3AAY. One section of a transistor transmitter.

Linear Power Amplifiers, ZL3BFR. Handy theory session.

Generating R.T.T.Y. Tones, ZL2AVF. For those interested in the mode.

Suppression of Transistor Power Supply Noise, ZL3BBO. He says that the wine is not necessary.

Diode E.F. and A.G.C. Circuit for Receivers, ZL4IC. Covers some interesting areas of receiver design.

Chatham Island DX-pedition, ZL1TU/C and ZL1H/C. Part two of the story.

"CQ"

August 1968—

Putting the Central Electronics 100V and 200V on 160 Metres, KHE1J. This author suggests that some of the older secondhand units will make good 160 metre rigs.

Results of the 1968 "CQ" World Wide DX (CW) Contest, WIWY. All the details for those interested in DX.

Signals from Space, W3ASK. Satellite DX can be satisfying.

Slew Scan Television. Part two of an article began in the July issue.

"CQ" Reviews the Swan 250C 6 Metre Transceiver, W2AEF. This is a new model of Swan's six metre transceiver and mainly discusses the improvements.

The 5-DEC Unit, W2AEF. This is a system of bread-boarding equipment simply by pushing the wire ends of components into holes in a board. Up to date I have not seen it in Australia.

Converting the Heath CB-1 to Six Metres, W6CWN/4. This article describes the conversion of a CB transceiver to six metre operation. Also includes the addition of a simple audio squelch circuit.

The Inductometer, W6SAL. The ingredients of a versatile antenna system to operate from 1.8 to 30 Mc., patterned after the AN/SRA33, makes use of a 35 ft. whip, a variable impedance matching transformer, loading coil and

s.w.r. bridge. It will work into random lengths of wire.

Australas Oscar, W3ASK. Australas Oscar, the fifth in a series of satellites designed and built by Radio Amateurs is due to be launched soon. This article discusses how its signals can be received and tracked, how its telemetry signals can be used for scientific experiments, and QSL cards obtained for space listener reports.

September 1968—

Herbert Hoover, Jr., W6ZH. 1903 to 1969. The Evolution of a Circulator Coupled Paramp, W6NLZ. The circulator is the key to success with parametric amplifiers. Noise figure about 1 db.

Remotely Antenna Tuning, W6BCQM. 1-2 r.p.m. motor and continuously variable capacitor produces do it yourself r.c.

Australas Oscar, W3ASK. The latest dope. "CQ" W.W.D. Contest Results. For the DX man.

An Automatic Transistor Checker, W2EY. Lamp type Go-No-Go indications.

Build a Complete Six Metre Station, WA-2NDM. Part one, small mobile valve job.

Receiver Sensitivity and Noise Figure, by W2EY. Do you confuse sensitivity and noise figure? If so, this is for you.

The Integrated Circuit Electronic Keyer, by GWN.

Modifying the Heath HP24 Power Supply for use with 8.0 Tubes, W2EY.

"CQ" Reviews the Heathkit SB-500 Two Metre Transceiver, W2AEF.

"DAS DL QTC"

The Journal of the German Amateur Radio Club, August 1968. This publication is of interest to those amateurs who can read German or can get the articles translated. In the August issue is an article on an s.b. transmitter for the h.f. bands by Hans VK3AOU (ex DL1EZ). The German society is frequently in the forefront of developments and some of their articles look quite interesting.

In the August issue is one by DL4W who describes how either a variable capacitor or a variable inductor (variometer) can be used to tune an L antenna to operate on either 80 or 40 metres. Perhaps some of the disposable equipment available out here would yield such components for use by VKs or perhaps a ferrite rod may give similar results.

Co-axial Fed L Antenna for 80 and 40 mX

This translation is pretty rough because it was done by someone who is non-technical and just dressed up a little by the writer.

"Once the inverted L type antenna was very popular. A normal pi network made it easy. I had one which because it consisted of 41 metres of 3.5 mm. phosphor bronze wire, I considered it too good to throw away."

"Upon converting to s.b. I found myself faced with a pi network which would only match over the range 40 to 120 ohms and this

did not match the 20 mX long open feeder of the inverted L. The question was, how to feed the antenna with 60 ohm (common impedance in Germany, designed for both 50 and 75 ohms) co-axial cable and still work in 80 and 40 mX bands.

Both 80 and 40 mX frequency bands were not considered, as experience had shown that a ground plane was superior to the L on the DX bands. The problem was solved elegantly by using odds and ends from the "bag of tricks". The circuit can be arranged in either of two ways. A fixed inductor and variable capacitor or fixed capacitor and variable inductor may be used. Using the fixed inductor-variable capacitor combination, I found that I could only obtain a low s.w.r. at one point in each band so I took a variable 6-36 microhenry inductor from an old Army transmitter. A capacitive divider was formed from values of 1 nF, and 80 pF in series across the antenna. The 80 ohm cable fed to the junction of the capacitors with the larger value and the grid dipper between the conductor and ground. The grid dipper showed that this combination covered the range 3-4.8 Mc. Because of the exceptionally high quality of the variometer the dynamic impedance of the variometer was the limiting factor. Because the impedance of the L antenna was in the region of 3K ohms, it was easy to tap it with a suitable point on one-third of twenty turns.

"The s.w.r. is now less than 1:0.5 in both the 80 and 40 metre bands and the harmonic suppression is in the order of 40 db."

"Experimenting showed this variometer to be useful up to input powers of about 150w, (r.f.) beyond which it needed special damping with a good insulator. The variometer is arc-over was likely to occur. For best results the variometer should be located at the end of the antenna with a very short feeder. My variometer was tuned remotely by a small motor and the feed should be through a substantial insulator."

"HAM RADIO"

Although I have been a reader of American magazines for over 20 years, I did not really note the name Jim Flak, WIDTY, until I was presented with a copy of a new Amateur magazine called "Ham Radio" which was published in New York, during March 1965. Your Publications Committee has now obtained copies of this new publication for the current year.

"Ham Radio" is similar in page size to "Q", "CQ" and "73" pages are roughly half the size of our own "Amateur Radio" and measure 5 1/4 x 9 1/4 inches. Issues at present average 100 pages.

I have been surprised recently by some of the content of one of the American magazines which appears to be very "anti-A.R.R.L." I think this sort of attitude is very unfortunate in a magazine and I am happy to say that Jim Flak's new publication does not seem to be "anti" anyone, he files his issues with as much technical information as he can in well written and informative articles with quite a lot of meat in them. The magazine is well organized from cover to cover, layout is neat and the printing is beyond reproach. The cover price is 60c, whereas the cover prices of the other mentioned above are 75c. This probably means that you can buy "Ham Radio" for less than the others and if you are interested, I would suggest that you contact the subscriptions manager of the A.R.R.L. Our copies will be reviewed in sequence.

January 1968—

V.H.F./U.H.F. Effects in Gridded Tubes, W6UOV. In all tubes the connecting leads have inductance and capacitance and at v.h.f./u.h.f. these sometimes cause trouble.

Solid State Circuits for Single Sideband, F. H. Bell. Discusses a number of circuits which are used by the manufacturers of commercial equipment.

MOSFET Converter for 20 Mc., W2BEGZ. The author favours the R.C.A. types 2N159, 2N140 and 2N141 and the 2N141 is probably the best. 2N347B and 2N347B in the oscillator mixer chain.

Stub-Switched Stub-Matched Antennas, by W2EY. The author shows how transmission line sections can be used to match antennas at one frequency and switch at another. Some practical systems are described.

Solid State Controlled Tuning, by K2ZSQ. Inductors which are varied by varying the current through a control coil. Very interesting technique; maybe the prices have fallen to "Amateur level" or they are available in disposals.

Some Notes on Cubical Quad Measurements, W4VY. Handy tips for those who may be contemplating the construction or adjustment of a quad.

Novel Linear for Two Metres, W4KAE. For those whose transmitters are of low output a linear with an input power of 30 watts will

START THE NEW YEAR RIGHT WITH SWAN EQUIPMENT

Engineered to out-last, out-perform, and out-satisfy all other makes.

Just ask the Amateur who owns one. Available ex stock.

- ★ SW260 TRANSCIVER (complete station)
- ★ SW350C TRANSCIVER
- ★ SW500C TRANSCIVER
- ★ SW250 TRANSCIVER—6 Metre
- ★ TV2 TRANSVERTER—2 Metre
- ★ POWER SUPPLIES
- ★ ACCESSORIES
- ★ ANTENNA

Please forward coupon below for descriptive pamphlet

W.F.S. ELECTRONIC SUPPLY CO.

12 BOWEN STREET,

NTH. PARRAMATTA, N.S.W., 2151

Name.....

Address.....

Model of interest.....

give those extra miles. Uses inductive divider input and toroidal output circuits.

"The Repair Bench." Larry Allen takes the beginner and any old-timer who feels he may learn a thing or two about the trouble-shooting routines on popular circuits.

Antenna and Relator Preventive Maintenance, WA1ABP. Most of us sit 'em and forget 'em. Allen says that the assumption that it is better to leave well alone. Ted Woolner suggests that the beam owner can increase the life of the signal squarer by some simple maintenance.

The DXer is catered for by such features as propagation predictions for the month. There is also a New Products section.

February 1969—

High Power Grounded Grid Linear, W8SAL. Two 3-600Z's in a high power linear.

Signal Detection in the Presence of Noise, WB8IOM. Some methods of resolving those signals you can hear but cannot resolve are given.

Converting a Vacuum Tube Receiver to Solid State, W1OOP. Some of the older receivers, which are very good mechanically, can be converted to achieve a more powerful performance from less power. 3C34B—old chassis—new motor!

Power Supplies for S.S.B., F. H. Belt. The author discusses the required characteristics for the various modes of operation.

Miniature Keying Paddle, K6RIL, VK1AU. In the October issue of "A.R.R.L." said "if you cannot get one made, make it away!" This article is the answer to that problem.

Sleeping Inverted Vee Dipole Antenna, W6NIP. A vee with a difference.

V.T.V.M. Modifications, W6HPH. Describes how to build in that ohmmeter supply, etc.

Analyzing Incorrect D.C. Voltages, Larry Allen. Meter readings cannot always be taken for granted. This article tells why.

Universal Transistor Preampifier, W2EZY. John describes a pre-amp. to improve receiver S/N ratio from 80 to 6 metres.

March 1969—

Design Data for a High Power V.H.F. Linear, E8DQY. 2 Kw. g.e. linear for two metres. Maybe the "Moonbouncers" could get permission for one of these!

High-Stability Solid State V.F.O., W5YFB. One of your variable capacitor from a Command set this may interest you.

IC Frequency Calibrator, K6KA. Using a 10L4, this calibrator uses an existing 100 Kc. crystal and voltage obtained from the filament line.

The Real Meaning of Noise Figure, K6MIO. Fully expanded; if I dropped to read every word, I'd never get this column written, more's the pity.

Miniature Monitorscope, WA3FIY. A 902A and a handful of solid state components and you are on your way.

Newest Two Metre Ground Plane Antenna, W3WZA. Some Australian Amateurs have been using five-eighths on 144 Mc. This author makes a case for seven-tenths.

Safety in the Ham Shack, Jack Darr and Alan James take it upon themselves to show the uninitiated where they can go wrong with the use of the lower bands and of a pair of conductors carrying high voltage.

Integrated Circuit VOX, W2EZY. Using 10L4s, John says it is a big improvement on older methods of using relays like the 10L4.

Propagation Predictions for March, WB8KAP. Continues his monthly feature.

Computers in Ham Radio, W6TOM. The author suggests that there is a need for such a device to take the drudgery out of it. I thought Amateur Radio was a hobby!

Repairing High Voltage Transformers, W6NIP. Suggests that you should have a spare throw-away job may be capable of reclamation.

Ham Notebook. One of the features. This month D.C. Crystal Switching, S.B.E. Linear Amp. tips and Co-axial Cable Connectors, etc., in good measure.

"QST"

A Direct Conversion S.S.B. Receiver, W1DAX. A recent "QST" article has revived an interest in the direct conversion method for radio reception. Simplicity with good performance are the advantages. This article describes an experimental receiver using a novel approach to the use of direct conversion for true single-sideband reception.

A Three Element Delta Loop Beam for Six Metres, W1ICP and K1QKV. Each side of the delta is several feet long and it seems that this type of antenna is a practical device

for the 10 and 6 metre bands; it does not appear to be nearly so practical for 20 metres where the elements become rather unwieldy.

Squelch Circuits, W4SKM. A review of principles and practical circuits.

Transistor Switching for the Micro-Tw, by W1JE. Modification to a popular c.w. keyer described in "QST" August 1967 and in the A.R.R.L. Handbook. Here the relay goes solid state.

Grinding Technique for Surplus Crystals, W6PBI. Using the technique described here, the author has been able to make large changes in frequency without loss of activity.

Receiver Sensitivity. What it means. How it is measured. W7TV. Was a sensitivity figure of so many microvolts for such-and-such signal-to-noise ratio tell you anything?

Microelectronic Key, K2ERL. Combined receiver and audio monitor, all built on to a "bug" type base.

Strays. "QST" gives Cliff Tait, ZL1AKL, "The Flying Kiwi" mention on p. 35. CH is touring the world in an Airtourer 115 (nee Vicia) aircraft which was built in N.Z. He operates from the plane on 80 metres.

A Simple Two-Transistor A.F.S.K. Generator, W2BRH. This a.f.s.k. generator for r.t.t.y. can be built for less than \$10. Its low cost should not be a disadvantage. It has good performance. The author's generator was given some grueling tests in the A.R.R.L. lab. regarding output frequencies and it was found that after adjustment, the generator described it was necessary to use a frequency counter which would count in tenths of a cycle to measure the generator's output as a test generator for your i.s.k. demodulator.

An Inexpensive Ten-Minute Timer, W1EZZ. Another of those solid state devices built into a 3 x 4 x 5 inch mini-circuit. It is designed essentially to warn the Amateur when to identify his station.

Modern Filter Design for the Radio Amateur, W2NMQ. For the filter bend.

Australis Oscar 5. Progress report. With pictures of Owen Mace, Richard Tonkin and Paul Gaud.

The Outstretched Hand, W1UED. Help in Amateur Radio for the handicapped.

"THE INDIAN RADIO AMATEUR"

August 1969. This is a magazine which will have a lot of interest to our readers and it is not my normal practice to review it because most of the technical content is reprinted from Indian journals.

The Indian Radio Society obviously has many handicaps. Although India has a very large population, the Amateur is relatively rare and they have difficulty in obtaining parts for construction and in obtaining the necessary facilities such as the number of languages spoken in the country. By publishing articles taken from overseas magazines and contributed by the local loyalists, the Amateur Radio Society of India do a great deal to advance the cause of Amateur Radio in India.

August 1969—

This issue is stated to contain over 40 feature articles. These articles, covering a very wide spectrum, should interest everyone.

Listed in Two Metre Amplifier, K0VQY. A monitor receiver using only two transistors.

An FET Regenerative Receiver for 8.5 Mc. and up, W6OSA. Two FETs will allow you to have the best of the lower band and the upper band.

Multi Channel F.M. Operation, W4TEVX. Adding relay crystal switching to commercial f.m. gear.

The Case for the Five-Eighth Wavelength Vertical, W2EZY. This is the vertical with the low angle of radiation. Used for many years by thousands of broadcasting stations world-wide.

The Genesis of Radio Reception, W1USM. A history.

An Introduction to Integrated Circuits, by W1AIFJ. Let's hope that an intimate relationship results.

R.F.Y. Tone Generator, W7FLC. Now you can mark and space up a storm.

General Purpose Good-Bad Transistor Tester, W6KKA. Unless it fits all your transistors are in excellent shape.

A Compact Two-Metre Transmitter, W4UOY. 2200 output, phone.

Making Use of Surplus Transistors, by W1AIFJ. There are some enormous bargains around.

Skylines for 160 Made Simpler, W1EZZ. 160 metre antennas from A to exhaustion.

The Triax, K6TSP. New gadget you should know about. What next!

400-100 Kc. Sweep Frequency Generator, W4WOC. Sweep 100 Kc. not Mc. This is for aligning i.f. strips.

"What Do You Think? K10XK. A special "73" metaphysical feature.

Leaky Lines, K1AGZ. Grumbles by Sam, er, Dave.

FM—A Guide for Automatic Dials, W5GVC. An other automatic key and a good one. Only two transistors.

FM—Can Maker, K2PTS. Are you missing out on the f.m. bandwagon?

The 8B100 on Six Metres, WB4CXL. It's possible. (How many more will respond to similar trouble-shooting?)

Measuring the Frequency of Unmarked Crystals, K1EUY. Different, simple ways of doing this.

Extra Class Study Course, Part VII, by the Staff. There is no excuse for failing the test if you read this.

New You Can Have A Deviation Meter, K8STM. Don't deviate too much.

Two Transistor 1500-mile Transmitter, K0VQY. Quarter watt QRP rig for excitement.

Long Circular Quads, W4AKA. For moonbounce work.

Measuring F.M. Receiver Noise Figure, by W6BHB. Taking the mystery out of this for the receiver.

Would You like to be a Broadcast Engineer? K2ULR. No!

Measuring the Amateur and the Coastguard, W6UKX. What happens when an Amateur passes along a distress call.

A Transistor Parameter Tracer, K2PUR. Useful, unless tubes come back again.

For Sale Are We Here For W6BHB. Sometimes, as we tune the bands, perhaps we wonder too. Plus a number of other features. Comments are mostly from "73" which has a prepared review on page 1.

September 1969—

A DX Curtain for Fifteen Metres, VE1TG. Most Amateurs have heard of the "Sterb" Curtain," not too many will own one. Gain 3-4 db. over a dipole.

Tunnel Diode—Theory and Practical Applications, W6SCG. Including a one transistor, solar powered transmitter.

The Marble Tee, by Thorpe. Methods of running a transmitter in parallel.

Uncle Will and News from Poudre Valley, K0VDL. In dialect yet.

Building a Solid State W1EXT. Good Lord another article on soldering.

Light Naturally Runs Down, K1CLL. A special scientific American type feature.

Keen Pick-up and Shielding, W2EZY/I. Keen interference.

WVW—Pioneer in Standards Broadcasting, W1AJAA. Perhaps you've heard the catchy tune.

Basic Theory and Applications of Transistors, W1AIFJ. Something you have always wanted to know.

Series Gate, Solid State, K5ZVF. Clipper.

Improving NC300 S.S.B. Reception, W1OOP. It was good, now it's better.

A.F.S.K. Generator, W1ESH. Crystal controlled, using digital ICs.

Transistor Transistor Aspirin, K0VQY. How to keep from Westernising your transistors. (Dead one's tell no tales.—Ed.)

Improvement of Phone Intelligibility by Base Clipping, by Ives. Discussion of base clipping.

Measurement of Meter Resistance. Making it possible to verbalise your meters.

Diode Stack Power Supplies—The Easy Way, K6KA. Instant operation of the Henry 2K and others.

Transistor Testing Techniques, W6KXJ. Testing with a v.o.m. without destruction.

WVW Transistor Tester, K0VQY. Work the world with this three-transistor rig.

Neutralising the HX10, W2PQG. Simple way to stabilise this rig.

More Transistor Modulation, DL5KS. Remember that a.s.b. is still on v.h.f.

An Audio Signal Generator, W6FOO. Two ICs.

Capacitor Usage and Electron Flow, WHMKW. Work with your capacitor and why?

What About FM? W5VZV. We'll have you on f.m. this year.

A Primer on Radio Propagation, W1AGEK. If signals really do bounce, this is how it works.

Measurement of Percentage of Modulation, by Granger. C.f. a.m. transmitter.

Measurement of Meter Resistance, Part VIII, Staff. Let's get cracking.

Big Signal—Good Looks, W1ATA. 3-4000 k.w. linear.

WVW Videon Camera for A.T.V., W6VCO. Isn't it time you tried a.t.v.?

Two More Transistor Testers, W6DZJ. Handy if you were bogfoul.

W4WOC Compressor, W1AIOC. Audio compressor using two FETs.



Sub-Editor: DON GRANTLEY

P.O. Box 222, Penrith, N.S.W., 2780
(All times in GMT)

The month of October has been a good one from a DX point of view, with some good openings occurring for the VK/ZL DX Contest. This event provided some very good openings on all bands, however, a little more activity from VK and ZL would have helped. I spent about half the allotted time each week-end and was very surprised to note the conditions on 15 metres also in, in fact I hardly shifted from 15 over the c.w. week-end.

These good conditions are prevailing at the present time, and Mac Hilliard reports that 10 metres has been wide open to Europe on occasions at 1000z, with early morning conditions on 10 being comparable to those of the 1957 era. Sunspot count for June showed an average of 102, with wide variations from a daily low of 26, to a high of 168. Forecasts for November and December is 91 and 89 respectively.

George Studd, ZL2AFZ, comments that the use of the ZL prefix is a definite boost in that country a much needed boost, he himself filled a log book in six days, working all continents in one hour. Similar conditions should prevail when we use the AX prefix next year.

Recently under the Awards heading I ran a short notice on the Lincoln Award and this has been raised as to whether or not Port Lincoln in S.A. should be eligible. Slew Foster atured on this.

The following are active from the Svalbard Archipelago, JW8MI, JW6QL, JW7UH, JW2QK and JW8DL. The first three are there for about a year, JW7UH being active on 1400z c.w. and 14190/195 s.s.b.

Stations active from Thailand at time of writing are HS1AF, HS2AF, HS3AF, HS4AF and HS5ML, all are putting out good signals on 15 metres s.s.b. at around 1800z.

UA0NM continues to be active on Fridays from 1800 to 2100 on 14175 s.s.b. He is in Asiatic Russia, from Zone 19. Also from the same area is UA0LJ who is usually on 14025 on c.w.

CE2AT is heard regularly working CE2ZN on 14185 s.s.b. Fridays at 2115z. QTH is South Shetland.

Here are some more "nets". The Pacific Inter-island net meets Mon., Wed. and Fri. at 0400 on 14330 with a KK6 as M.C. The South East Asian net meets Sat. at 1200 on 14230. World DX Round Table operates 14270 s.s.b. Wed. and Sat. at 0500 to 0600z with WASUHR in the chair.

The VU0 prefix in use by Indian Amateurs for the month of October was in Commemoration of the late Mahatma Gandhi. QSLs for these stations to be sent to Box 6588, Bombay.

110ETN is good only for the prefix hunters, frequencies are 14180 and 21345 s.s.b. QSL to Box 66, Catania, Sicily.

MID is active daily 14100, 14150, 14180 s.s.b., and some 31 M.C. operation. No times are given and Giovanni can speak French but very little English. However, if you do hook him and want a QSL, send to IIMKN with I.R.C.

The OG prefix had recently been special calls issued for the SAC contest by the OH authorities. They count for the prefix hunters only.

FR7PZ/E which has been active for the past month is at Europa. OP is Maxime who is given the QRT at the end of October. All QSLs to Box 5, St. Clotilde, Reunion Is., Indian Ocean.

KHNH/Kure from Nov. 10 to Nov. 14, requests that all QSLs be sent to KHNH, Kure DX-post, 1001, Kitter Dyer, Honolulu, Hawaii, 96818, U.S.A.

5B4ES, another for the prefix hunters, is active from 2100 to 2200z on 14180 s.s.b. through Amateur Radio Club, Nicosia, Cyprus. His QSLs go to the International Short Wave League which is now located at 1 Grove Road, Lynton, Glos., England, GL15-5JE.

Did you work LT0ETN during the period Sep. 26 to 28? Then you are eligible for the LYNA Award medal for which you apply to Sezione ARI, Box 366, 95100, Catania, Sicily, with 15 IRCs. Also awarded for working any time.

419DX is another for the prefix hunters. He was UA9AN and operators from UA9KAI and UA9KAK operating from the South Ural Mountains during the "CQ" Contest.

Prefix hunters are really being catered for, here are a couple more: PZ0AA from Surinam Trade Fair recently, QSL to Box 366, Para-

maribo, Surinam. WC4GSC from Ogeechee Exhibition, Statesboro Georgia. QSL to W4DQD. Also E10RTS from RDS scientific exhibition in Dublin on Oct. 21 to 25.

YB1BC still very much active and putting a massive signal into VK2. Barry VK5BS has apparently worked the Pacific and the QSL return is very prompt if sent to Box 288, Bandung, Indonesia.

There has been little or no operation from Qatar lately, but ODSBZ has plans to go there late Nov. or early Dec.

ZD3JY is active from South West Africa on 2810z but has requested that he be sent to him at Box 5639, Windhoek, U.S.A.

From the Long Is. DX Assn. bulletin comes an item which will be of interest mainly to S.W.A.'s and covers the area of BY1F, both are active, and both say QSL via Radio Peking. It states that after sending your QSL to Radio Peking, you will receive newspaper monthly. You certainly will, and I suggest that you ignore them and don't give them the opportunity to use Amateur Radio as a propaganda outlet.

Still a few more nets. The YL-SSB net covering Oceania meets 14335 on Sat. from 0600z. Maritime net meets 11380 daily from 0600. Arganias net 1440z Tues and Thurs. 0930. CHC FHC net on 14340 daily from 1800, and on 7070 Sun. 1000z. Royal Navy ARS 2720 on Wed. from 1800. Finally, the British Commonwealth net meets daily on 21354 or 14285 from 1430 with W1PA as net control, and usually consists of service personnel.

LA3P/MK is often heard coming in 5 by 9 into VK2. QSL address for him is to his home address, Knut Gjertsen, Lallavold 2, Lofterod, Sandjord, Norway.

I mentioned at the start of these notes that there has been much increased activity on 10 metres. Some of the calls logged, heard or worked in VK and ZL over the past few weeks are DU1FH, UG6GM, UL7OA, VS8MB, VU2DK, SW2AF, SQ0CQ, EABDY, HV3SJ, KG6A, KP4CDR, KV4FZ, LA0AD, MP4BIS, MP4DIA, TR8DG, UD6AFO, VK9BB, VP8HZ, YN2JS, 8PAH, XW8CS, UA35U, 4STWA, 6MD1Q.

To go lower in the spectrum, 80 metres there has been quite an upsurge in activity. In the interests of space, I will quote some of the prefixes which have been logged or worked on both modes in VK and ZL over the past month. TI2, DJ8, DJ7, 11, H89, PA0, ON4, DK3, LA4, CP2, CT2, PG7, Y01, 4U1, 4Z4, OA4, OD5, 5Z4, OH3, 5Y1, Y3, 9Y4, JA, WA6, W1, W2, F3, F2, Y9, LIZ, G8, OH1, OH3, G2, F9, LU4, VE7 and many other W call areas.

Despite the good conditions, there is not a great amount of DX news this month. However, I would once again remind those interested, that the Pacific DX net broadcast a very fine bulletin of DX news at the start of their Friday evening session at 0630z on 14270. Look for net contacts, KH6GJ.

Some time ago I mentioned the use of the Z following the numeral in certain DU calls. Here is a list of stations together with their QSL managers: DU1ZAA/KIHT, DU1ZAB/WUTXP, DU1ZAC/K3MOV, DU1ZAE/W4NWR, DU1ZAF/PG1TV, DU1ZAG/WB6GF, DU1ZAH/W48US, DU1ZAI/KA6AP, DU1ZAJ/W48US, DU1ZAN/WIGL, DU1ZAW/W3EIV, DU1ZAD/W3MOV.

QTH SECTION

(By courtesy of the ISWL)
AZCAU-J. Large, Box 200, Francistown, Botswana, Africa.

CP1GN-U.S. Embassy, La Paz, Bolivia.
CZ1JW-J. Wirth, C/o. OTC, Nauru Is., Central Pacific.

CE0AE-Op. John, Det 517, APO, New York, N.Y. 09877, U.S.A.

DK1KY-E. Stammerberger, 5 Sauerbrucher, 8630 Coburg, West Germany.

FSPE-E. Ermis, Ferme Boulouche, 32 Lectoure, France.

FM7W0-B.P. 287, Fort de France, Martinique, French W.I.

FG7XL-B.O. 109, Pointe-a-Pitre, Guadeloupe, F.W.I.

HB0AFM-Box 282, 8040 Zurich, Switzerland.
JT1AK-Box 99, Ulan Bator, Mongolia, Asia.

KCSEB-Box 94, Ponape, East Caroline Is., 69941, Pacific.

KCSSE-E. Sugiyama, Koror, Palau Is., West Caroline, 99940.

LA5K0-Postfack 150, Slependen, Norway.
LU4VL-Atto 121, Allen, Rio Negro, Argentina.

MP4BIS-Box 155, Manama, Bahrain, Arabian Gulf.

MP4BHL-Box 444, Bahrain.
OH2AM-Box 6015, Helsinki 40, Finland.
P39BG-C/o. Trans World Radio, Bonaire, Netherlands Ant.

P39VL-Box 60, Curacao, Netherlands Ant.
PY4AP-CP 484, Belo Horizonte, Minas Gerais, Brazil.
TR8DC-Guy Delas, Box 356, Libreville, Gabon Rep.

VE2AFC-BP 382, Quebec 4, P.Q. Canada.
VS6AFC-C/o. HKARTS, Box 541, Hong Kong.
VR3FT-L. Higginbotham, Box 3722, Samabula, Fiji.

W3WVU/YB6-3030 Marshall Rd., Pittsburgh, Penn. 15214, U.S.A.

YJ8BM-J. MacIntyre, Dept. of Telecom, Santo, New Hebrides.

YJ8RG-N. Graham, C/o. P.O. Vila, New Hebrides.

ZE1CY-Bob Furzer, Box 738, Gwelo, Rhodesia.
ZS6LW-Box 838, Germiston, Rep. of South Africa.

ZS4LS-Nick Henwood, Box 448, Nyeri, Kenya.
5V4DB-BP 123, Lome, Togo, Republic, Africa.

The prefixes CSA-CSZ have been allocated by the I.T.U. to the Principality of Andorra. Formerly EX1, that prefix was unofficial and in reality belonged to Brazil.

Unfortunately, I will have to close these notes here this month. However, I will have a full screed for the next issue. My thanks this month to George ZL2AFZ, Mac Hilliard, Maurice Cox, Geoff Watts DX News Sheet, LIDXA, Barry VK5BS, ISWL, Jack VK3IAK, Ernie Luff, Bernard Hughes and Stewart Foster of England. Until the next time, 73, Don L2022.

GMT?

Solve the problem the easy way with a

"SOLARI" 24-HOUR DIGITAL CLOCK

2134

Now available, a compact attractively styled direct read-out Digital Clock for the modern office, home or radio shack. Ideal for logging under 24-hour system, either GMT or local times. Large, easy-to-see figures on direct-read flaps give the correct time, minute by minute—no hands to misread. 220-240 volt 50 c.p.s. synchronous motor, simple time re-setting; lightweight, unbreakable plastic case 7" wide, 3 3/4" deep, 3 3/4" high, in beige or light grey. Also available in 12-hour type for general home use. State type and color required.

Price only \$32 inc. S.T. + postage
(Packed weight, 2 lb.)

IDEAL CHRISTMAS GIFT!

Available from:

Bail Electronic Services

60 Shannon St., Box Hill Nth.,
Vic., 3129. Telephone 89-2213

INTRUDER WATCH NOTES

A. W. Chandler, VK3LC, has replaced M. P. Davis, VK3JAG, as Victorian State Intruder Watch Co-ordinator.

STATE INTRUDER WATCH CO-ORDINATORS

VK3—W. H. R. Treloar, VK3BZF, 23/8 Puller-st., Woodhams, N.S.W. 2025.
VK3—A. W. Chandler, VK3LC, 1534 High St., Glen Iris, Vic., 3146.
VK4—C. E. Kenny, 19 Lithgow St., Wynnum North, Qld. 4178.
VK5—John Bulling, VK5KX, 297 Goodwood St., Kings Park, South Aust., 5034.
VK6—C. Allen, 283 Amelia St., Balga, West. Aust., 6051.
VK7—D. H. Kelly, VK7DK, 56 Upper Brougham St., Launceston, Tas., 7250.

PROVISIONAL SUNSPOT NUMBERS

OCTOBER 1969
Dependent on observations at Zurich Observatory and its stations in Locarno and Arosa.

Day	R	Day	R
2	54	16	33
2	101	17	38
3	98	18	43
4	92	19	48
5	103	20	87
6	117	21	102
7	120	22	107
8	122	23	124
9	89	24	133
10	78	25	137
11	58	26	142
12	60	27	138
13	47	28	121
14	55	29	113
15	46	30	80

Mean equals 80.9.

Smoothed Mean for April 1969: 103.0.

—Swiss Federal Observatory, Zurich.

SHOUT YOURSELF A XMAS BOX

that will last the whole year!

A subscription to "Break-In"
official journal of N.Z.A.R.T.
will cost you only \$2.35.

Send it to: Federal Subscription Manager,
Wireless Institute of Australia,
P.O. Box 87,
East Melbourne, Vic., 3002.

* TRANSISTORISED TRANSMITTERS

* RECEIVER DESIGN

* INSTRUMENTATION

* MODULATED LIGHT COMMUNICATION

* THE SUPER WORMTURNER

* REAL BOOK REVIEWS!

* PITHY COMMENTS ON EVERYTHING

All this, and more, in the E.E.B.

Send for Sample Copy

THE AUSTRALIAN E.E.B.

P.O. Box 177, Sandy Bay, Tasmania, 7005.

Swan Electronics Service Co.

Accredited Distributor for

Swan, Hallcrafters, etc., Receivers
and Transmitters

Specialised Service on all

Swan Transceivers

14 GLEBE ST., EDGECLIFF, N.S.W., 2027. Ph. 52-5465

REPAIRS TO RECEIVERS, TRANSMITTERS

Constructing and testing: xtal conv.,
any frequency; Q5-ers, R9-ers, and
transistorised equipment.

ECCESTON ELECTRONICS

146a Cotham Rd., Kew, Vic. Ph. 80-3777

VHF NOTES

(Continued from Page 31)

extended phase array or 13 element yagi 50 ft. high, ERCC cascade front end in converter. The tunable i.f. range of 27 to 29.5 Mc. is utilised in his Yaesu Vnuen FR100B receiver which is used for all three bands. The modulator has Class B zero bias 807s with high level clipping and filtering. This latter Mick considers essential, and he and others. Not long ago he spent 12 months at Tantanoola in the South East of S.A. and was keen enough to lug all his equipment down there with excellent results.

Plans for the future include working VK8 on 144 Mc., forward scatter experiments on 52 Mc., and possible operation on 578 or 1296 Mc. If the past is any guide, it is certain Mick will achieve all these things, and Amateur Radio will be the richer for it.

NEW ZEALAND

Our friends across the Tasman in New Zealand are holding their V.h.f. Field Day on Saturday and Sunday, 6th and 7th December. Amateurs in VK could well keep an ear on the bands for inter-country contacts. ZL1BPA and ZL1AJP have had another two-way contact on 3800 Mc., this time over a distance of 86.25 miles, contact was loud and clear using fm. Further experiments are being undertaken to extend this distance.

John ZLIAZR continues his Moonbounce skeeds with Kjell SMITAE and Dick KOMGS. In a recent letter he says that he is replacing his present Earth-Moon-Airial earth (eight 6/8 skeleton slots) with eight long yagis which feature high feed impedance driven elements. The new aerial will have about 32 db. gain compared with the 30 db. given by the old array. John says that it is most necessary to use high impedance in the stacked yagi arrays for it is almost impossible to drive low impedance units in large arrays.

The ZL3 144 Mc. beacon has received Post Office approval, and with every hope of being operational by the time these notes are read. No details of frequency as yet, perhaps by next issue.

This being my first issue of notes, and having very little idea what space a typewriter takes compared with the printed word, will wait and see if I have been too eloquent or not. I acknowledge with thanks information supplied by Peter VK2ZCP, Peter VK3ZYU, Mick VK5ZDR, "Break-In" and "Spectrum", the latter two being New Zealand publications.

For future pages I am looking for information of national interest, something which can be read and appreciated in all States. Anyone may contribute, but all information will be re-edited, and acknowledgments given near the end of the v.h.f. page. Plenty of notice regarding contests, field days and other events will ensure some publicity will be given prior to the date of the event. Lengthy writing about any particular subject must of necessity risk fairly severe re-editing to keep it interesting to all, and save space.

I look forward to a happy period with you all. Traditionally, I always close my notes, wherever they are printed, with a thought for the month: "In democracy, the votes of the vicious and stupid count. But under any other system they might be running the show." A Merry Christmas to all, B3, Eric VK5LP ("The Voice in the Hills").

W.I.A. V.H.F.-C2

New Members

Cert.	Call	Confirmations
60	VK3ZOO	52 Mc. 144 Mc.
61	VK1VP	— 100
62	VK3ZOP	— 100
63	VK4ZOC	— 178
64	VK3ZKP	— 100
65	VK3ZBB	— 109
67	VK3ZKW	161

FEDERAL AWARDS

AUSTRALIAN D.C.C.C. COUNCILS LIST

Deletion: EA9 Ifni. Only contacts made prior to 12/5/69 will be credited. Contacts with stations located in the former Spanish territory of Ifni made after that date will be counted towards the Morocco Listing.

All D.C.C.C. members who have claimed Ifni have had their scores amended as necessary.

—Geoff Wilson, VK3AMK,
Federal Awards Manager.

CONTEST CALENDAR

6th Dec. '69 to 11th Jan. '70: Ross A. Hull V.h.f. Memorial Contest.
6th/7th Dec.: CHC International DX Contest (c.w.).
13th/14th Dec.: CHC International WX Contest (s.s.b.).
7th/8th Feb.: John Moyle National Field Day Contest.
7th/8th Feb.: 36th A.R.R.L. International DX Competition (1st phone week-end).
21st/22nd Feb.: 36th A.R.R.L. International DX Competition (1st c.w. week-end).
7th/8th March: 36th A.R.R.L. International DX Competition (2nd phone week-end).
21st/22nd March: 36th A.R.R.L. International DX Competition (2nd c.w. week-end).

HAMADS

Minimum \$1 for forty words.
Extra words, 3 cents each.

HAMADS WILL NOT BE PUBLISHED UNLESS
ACCOMPANIED BY REMITTANCE.

Advertisements under this heading will be accepted only from Amateurs and S.w.'s. The Publishers reserve the right to reject any advertising which, in their opinion, is of a commercial nature. Copy must be received at P.O. 36, East Melbourne, Vic., 3002, by 5th of the month and remittance must accompany the advertisement.

DECEASED Amateur's Equipment: 1 Yaesu Museen FR500 Receiver, 1 Yaesu Museen FL50 Transmitter, 1 Yaesu Museen FV50 Transistorised V.F.O., 1 home constructed aerial tuning unit plus an indicator with 0-100 microammeter. 1 Aiwa Crystal push-to-talk Mic. This comprises a complete station having either independent or transceive operation plus the outboard V.F.O. for separate transmitting. The transmitter has VKO for plug-in crystals with between 5 to 7 Kc. adjustability. Firm offers please by mail, preference to a purchaser taking all. All offers will be replied to, your phone number an advantage. Write to Bob Thompson, 91 Lucan Ave., Aspley, Qld., 4034.

FOR SALE: Central Electronics 20A Exciter, 160 through 10, in excellent condition, will drive 813 or similar tubes. SSB, SSB, complete set, modified for above exciter, \$25. BC4548 general purpose v.f.o., \$20. T433JR Triband Beam, weather proofed, \$20. Type 101. Trans/Rec. c.w. modulator and key, in-built power, 800, 400, 400, or 80, c.w. base or mobile, ant. spares, etc., instruction manual, \$70. C.R.O. University 3 inch, mint condition, \$50. N.W. Fletcher, VK2DQ, 8 Seaview St., Balgownie, N.S.W., 2093. Phone 94-1039.

FOR SALE: Gecoso G222 Transmitter and G209 Receiver, Panda 10/15/20 xlm Beam complete with prop. motor with transformer rotor in covered housing. Best offers to Ken Meallin, VK3NJ, 60 Caroline St., South Yarra, Vic., Phone 68-1032, home 26-5515.

FOR SALE: Hallicrafters live-band, s.s.b., c.w. Transceiver, Model SP18, complete with 1000 watt power supply, VOX, PTT, 125 watts p.e.p. input, instruction manual, \$350 o.n.o. VKIAN, 37 Ingalls St., Garran, A.C.T., 2605. Phone (062) 81-5065.

FOR SALE: R.C.A. Beat Frequency Oscillator, ex P.M.G. Labs., \$15. A. G. Fletcher, VK3VX, Phone 61-1853 (Mails).

FOR SALE: Yaesu Museen FT-400 Amateur Communications Receiver. In as new, immaculate condition. Only a few months old. \$295. Lee Andrews, 49 Lord St., Roseville, N.S.W., 2069, or Phone 46-1022 after 6 p.m.


SELL: AVO Model 8 Multimeter, 20,000 ohm/volt, accurate cable calibration, \$40. 175 Frequency Meter, 55 Mc. to 1000 Mc. Telemax u.h.f. version of Bendix 221, as new, \$80. J. Mcleiver, 40 Beanga St., Greenslopes, Brisbane, 4120. Phone 97-6036.

S.W.L. Specifications: BC453 with power supply, \$25. Panoramic Adaptor, 3A-520, \$70. Six Ham Band, accurate Cable Coverage Receivers, \$25 to \$100. All gear in good going order. H. Roach, 28 Foote Avenue, Glenhenty, Vic., Phone 58-3757.

WANTED: 1 Edystone "640" Receiver with at least the r.f. section and xtal filter intact. Station condition and price. Write to R. F. Lloyd, 171 Chandler Road, Keon Park, Vic., 3073. Preferably Melbourne area.

HY-GAIN AMATEUR ANTENNAS

Fully Imported
from U.S.A.

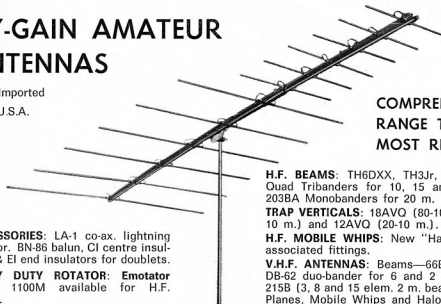

**COMPREHENSIVE
RANGE TO SUIT
MOST REQUIREMENTS**

ACCESSORIES: LA-1 co-ax. lightning arrester. BN-86 balun, CI centre insulators & EI end insulators for doublets.

HEAVY DUTY ROTATOR: Emotator Model 1100M available for H.F. beams.

H.F. BEAMS: TH6DXX, TH3Jr, TH3Mk3 and Hy-Quad Tribanders for 10, 15 and 20 m.; 204BA, 203BA Monobanders for 20 m.

TRAP VERTICALS: 18AVQ (80-10 m.), 14AVQ (40-10 m.) and 12AVQ (20-10 m.).

H.F. MOBILE WHIPS: New "Hamcat" Whips and associated fittings.

V.H.F. ANTENNAS: Beams—66B six elem. 6 m., DB-62 duo-bander for 6 and 2 m.; 23B, 28B and 215B (3, 8 and 15 elem. 2 m. beams). Also Ground Planes, Mobile Whips and Halos.

BAIL ELECTRONIC SERVICES, 60 Shannon St., Box Hill North, Vic., 3129. Ph. 89-2213

Rep. in N.S.W.: A. J. ("SANDY") BRUCE SMITH, 11 Ruby Street, Mosman, N.S.W., 2088. Telephone 969-8342

BRIGHT STAR CRYSTALS

**FOR ACCURACY, STABILITY, ACTIVITY
AND OUTPUT**



Our Crystals cover all types and frequencies in common use and include overtone, plated and vacuum mounted. Holders include the following: DC11, FT243, HC-6U, CRA, B7G, Octal, HC-18U.

THE FOLLOWING FISHING-BOAT FREQUENCIES ARE AVAILABLE IN FT243 HOLDERS:

6280, 4095, 4535, 2760, 2524 Kc.
5.500 Kc. T.V. Sweep Generator Crystals, \$7.25;
100 Kc. and 1000 Kc. Frequency Standard, \$17;
plus Sales Tax.

Immediate delivery on all above types.

AUDIO AND ULTRASONIC CRYSTALS—Prices on application.

455 Kc. Filter Crystals, vacuum mounted, \$13 each plus Sales Tax.

ALSO AMATEUR TYPE CRYSTALS—3.5 Mc. AND 7 Mc. BAND.

Commercial—0.02% \$7.25, 0.01% \$7.55, plus Sales Tax.

Amateur—from \$6 each, plus Sales Tax.

Regrinds—Amateur \$3, Commercial \$3.75.

CRYSTALS FOR TAXI AND BUSH FIRE SETS ALSO AVAILABLE.

We would be happy to advise and quote you.

New Zealand Representatives: Messrs. Carrel & Carell, Box 2102, Auckland.

Contractors to Federal and State Government Departments.

BRIGHT STAR RADIO

LOT 6, EILEEN ROAD, CLAYTON, VIC.

Phone 546-5076

With the co-operation of our overseas associates our crystal manufacturing methods are the latest.



DURALUMIN ALUMINIUM ALLOY TUBING

**IDEAL FOR BEAM AERIALS
AND T.V.**

★ LIGHT ★ STRONG
★ NON-CORROSIVE

Stocks now available for
Immediate Delivery

ALL DIAMETERS — 1/4" TO 3"

Price List on Request

STOCKISTS OF SHEETS—

ALL SIZES AND GAUGES

GUNNERSSEN ALLEN METALS

PTY. LTD.

**SALMON STREET,
PORT MELB'NE, VIC.**
Phone 64-3351 (10 lines)
Telegram: "Metals" Melb.

**HANSON ROAD,
WINGFIELD, S.A.**

Phone 45-5021 (4 lines)
Telegram: "Metals" Adel.



REALISTIC PERFORMANCE REALISTIC PRICE



REALISTIC **DX150** **ALL SOLID STATE—4 BAND** **COMMUNICATIONS RECEIVER**

A big professional looking set that makes exciting news for amateurs... the DX150 gives realistic reception on SW/CW/SSB/AM—Broadcast bands; obsoletes tube receivers with their warm-up delays; banishes dependence on AC main power... the DX150 will run on dry cells if current fails or is not available; will operate from a car's cigarette lighter or any 12V DC service. 240V AC power supply is built-in, of course.

Over 30 semi-conductors—Product detector for SSB/CW, plus fast and slow AVC—variable pitch BFO—illuminated electrical bandspread fully calibrated for amateur bands—Cascade R.F. Stage—ANL for RF and AF—Zener stabilised—OTL audio—illuminated "S" meter—Built-in monitor speaker plus front panel jack for external (optional) matching speaker.

Attractive silver extruded front panel, solid metal knobs, grey metal cabinet, size 14 1/4" x 9 1/4" x 6 1/2" —... a truly Realistic performer at a realistic price.

\$229.50

**Brings in the
whole wide world of
SW/CW/SSB/AM—
Broadcast**

**240V AC or 12V DC
operation.**

CONSULT YOUR LOCAL RADIO DEALER, OR

MAIL THIS COUPON *today*

Please forward free illustrated literature and specifications on Realistic.

Name.....

Address.....



(A unit of Jacoby Mitchell Holdings Ltd.)
375 EASTERN VALLEY WAY, ROSEVILLE, N.S.W.
Cables and Telegraphic Address: 'WESTELEC.'
Sydney. Phone: 40 1212

Hy-Q ELECTRONICS

*Australia's
largest
independent
crystal
manufacturers*

EXTEND THEIR PRODUCT RANGE TO INCLUDE

- Fundamental and overtone crystals from 1 MHz. to 125 MHz.
- 10.7 MHz. crystal filters for 25 & 30 KHz. systems.

SEND FOR FULL DETAILS
IF YOU HAVE NOT ALREADY
RECEIVED THEM

Hy-Q Electronics

Hy-Q ELECTRONICS PTY. LTD.

10-12 ROSELLA STREET,
P.O. BOX 256,
FRANKSTON, VICTORIA 3199.

Telephone 783-9611. Area Code 03.

Cables: Hyque Melbourne


Telex: 31630

STOP RUST OUTDOORS TWO YEARS... OR MORE!

Lubricates Penetrates Stops Rust

DRY YOUR ELECTRICAL SYSTEMS
with **LPS** — the NON-GREASY ONE

**STOPS
Squeaks!**

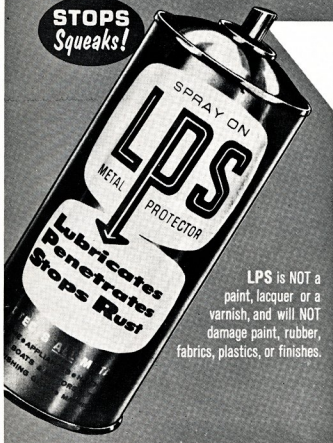

LPS is NOT a paint, lacquer or a varnish, and will NOT damage paint, rubber, fabrics, plastics, or finishes.

Displaces Moisture Fast!

TECHNICAL INFORMATION

Physical Properties:

LPS 1

Less than 0.0001 inch non-greasy molecular film with capillary action that spreads evenly and easily to seal out moisture at very low cost.

Rust Inhibitor: Protects all metals from rust and corrosion.

Water Displacing Compound: Dries out mechanical and electrical systems fast.

Lubricant: Lubricates even the most delicate mechanisms; non-gummy, non-sticky; does not pick up dust or dirt.

Penetrant: Penetrates to loosen frozen parts in seconds.

Volume Resistivity per ASTM D-257: Room temperature, ohm/cm.; 1.04 x 10¹¹.

Dielectric Constant per ASTM-877:

Dielectric Constant 2.11, Dissipation Factor: 0.02.

Dielectric Strength per ASTM D-150:

Breakdown Voltage 0.1 inch gap, 32,000 volts.

Dielectric Strength volts/inch, 320,000 volts.

Flash Point (Dried Film), 900 degrees F.

Fire Point (Dried Film), 900 degrees F.

TESTS AND RESULTS: 950 degrees F.

Lawrence Hydrogen Embrittlement Test for Safety on High Tensile Strength Steels: Passed. Certified safe within limits of Douglas Service Bulletin 13-1 and Boeing D6 17487.

Mil. Spec. C-16173 D-Grade 3, Passed.

Mil. Spec. C-23411, Passed.

Swiss Federal Government Testing Authority for Industry: Passed 7-Day Rust Test for acid and salt water. Passed Weiland Machine Test for Lubricity as being superior to mineral oil plus additives.

LPS Products conform to Federal Mil. Specs. C-23411 and/or C-161730



Sole Agents:

ZEPHYR PRODUCTS

HOW LPS SAVES YOU TIME AND MONEY

1. LPS PROTECTS all metals from Rust and Corrosion.
2. LPS PENETRATES existing rust—stops it from spreading.
3. LPS DISPLACES moisture on metal—forms fine protective film.
4. LPS LUBRICATES even the most delicate mechanisms at extreme temperatures.
5. LPS PENETRATES to free rust frozen parts, nuts, bolts, etc.
6. LPS PREVENTS equipment failures due to moisture (drives it out).
7. LPS LENGTHENS LIFE of electrical and electronic equipment—improves performance.
8. LPS RESTORES equipment damaged by water contamination and corrosion.
9. LPS PENETRATES AND PROTECTS plated and painted metal surfaces.
10. LPS PROTECTS metals from salt atmosphere, acid and caustic vapours.
11. LPS LOOSENS dirt, scale, minor rust spots and cleans metal surfaces.
12. LPS ELIMINATES squeaks where most everything else fails.

PTY. LTD., 70 BATESFORD ROAD, CHADSTONE, VIC., 3148. Phone 56-7231

INDEX TO VOLUME 37-1969

ANTENNAE

Antenna Farming on 7 Mc.	Oct. p.10
Design of a Three-Band Beam for 28, 21 and 14 Mc.	Sep. p.14
Expanded Lazy-H Antenna	Aug. p.10
Moon Bounce	Jul. p.15
More on the Single Loop, Tri-band Cubical Quad Beam Element	Dec. p.20
The DJ4VM Multiband Quad	May p.13
The Ferrite Balun	Apr. p.9
The World with a Triangle	Apr. p.10
The ZE4J Special 3-Element Tri-band Beam	Jun. p.8

AUDIO AND MODULATORS

Economy Speech Compressor	Apr. p.12
Useful Circuits using Computer Board Transistors	Sep. p.10

CONTEST RULES AND RESULTS

John Moyle Memorial National Field Day Contest:	
1969 Rules	Jan. p.17
1969 Results	Jun. p.16
1970 Rules	Dec. p.25
Remembrance Day Contest:	
1969 Rules	Jul. p.20
1969 Results	Nov. p.20
Results of VK3 Division 160 Metre Contest	Jan. p.23
Ross Hull Memorial V.h.f. Contest:	
1968-1969 Results	May p.17
1969-1970 Rules	Oct. p.15
VK-ZL-Oceania DX Contest:	
1968 Results	May p.16
1969 Rules	Aug. p.22

INSTRUMENTS

A C.W. Clipper-Filter using FETs	Jul. p.18
A FET Gate Dip Oscillator	Jun. p.14
See Technical Correspond.	Aug. p.21
Compact Multi-Purpose Test Instrument	Oct. p.11
Diddle Dah Dah Dah Dah Ditt!	Nov. p.6
Electronic Keyer	Jun. p.7
Frequency-Independent Directional Wattmeter, and an S.w.r. Meter	Nov. p.14
Modifications to the No. 10 Crystal Calibrator to use 3 Volt Filament Supply	Sep. p.16

MISCELLANEOUS

Amateurs Locate Missing Aircraft	Sep. p.18
Amateur Radio and the 1968 Blue Mountains Bushfires	Feb. p.17
Aust. D.X.C.C. Countries List	Jan. p.14
Aust. DX Cent. Club Award	Jan. p.13
Australis Oscar 5:	
Launch Imminent	Nov. p.19
New A.R. Satellite Group	Jul. p.25
Observations from Australis Oscar 5	Dec. p.19
Progress Report	Dec. p.18
Satellite Ready for Launch	Oct. p.7
Aust. V.h.f. Cent. Club Awd'd Call Signs in the Territories	Jan. p.13
Federal Constitution Change of W.I.A.	Sep. p.25
Geelong Radio & Electronics Society's New Club Rooms	Aug. p.21
Intruder Watch Gets Into Gear	Jun. p.14
"It"	May p.15

I.T.U. Conference—7/6/71	Aug. p.14
New Circulation Policy	Aug. p.24
Notes from Federal Repeater Secretariat	Nov. p.17
Notes of 1969 N.F.D.—As seen by VK2AAH/P Group	Jul. p.21
Opening Address for 1969 Remembrance Day Contest	Oct. p.18
Please QSL OM	Aug. p.21
Rhodesian Beacon ZEI3ZA Back on the Air	May p.27
Special Call Sign Granted by P.M.G.	Aug. p.7
The Questionnaire:	
Some Prelim. Observations	Jan. p.22
A Progress Report	Feb. p.19
Some Further Progress	Mar. p.7
The 1969 Federal Convention—A Report	Jun. p.18
Tourist Commission Provides QSL Cards	Aug. p.7
Trade Review: H.M.V. "Kimberley"	Jan. p.12
Vic. Div. 160 Mx Field Day	Oct. p.19
W.I.A. Cook Bi-Cent. Award	Aug. p.7
W.I.A. Fed. Ex. 1969 Annual Report to Federal Council	May p.20
W.I.A. Fed. Pres. Speech to N.Z.A.R.T. Conference	Jul. p.22
W.I.C.E.N. Exercise by VK3 North-Western Zone	Mar. p.17

POWER SUPPLIES

The 122—S.s.b. and Power Supplies	Jan. p.11
High Voltage Regulators	Dec. p.15

RECEIVERS

A C.W. Clipper-Filter using FETs	Jul. p.18
An Experimental 455 Kc. I.F. Strip	Mar. p.5
A Modification to the Trio 9R59DE Receiver	Apr. p.11
A Solid State Amateur S.s.b. Receiver, Part One	Oct. p.13
Converting the AR88 for S.s.b.	Jul. p.7
Detecting V.h.f. Signals too Weak to be Heard	Jan. p.18
Finding True Receiver Sensitivity	Jul. p.12
General Coverage High Frequency Converter	Jan. p.5
Improved F.M. Operation	Apr. p.13
Improving Eddystone EC-10 as a Tunable I.F. for V.h.f. Converters	Jun. p.9
Project—Solid State Transceiver:	
Part Three	Jan. p.8
Erratum to Part Three	Mar. p.10
Part Four	Feb. p.13
Part Five	Mar. p.8
Part Six	Apr. p.7
Part Seven	May p.10
Part Eight	Jun. p.10
Part Nine	Aug. p.8
Part Ten	Sep. p.7
Solid State Coupling Methods	Feb. p.9
The W5OMX Com. Receiver	Mar. p.11
The 122—S.s.b. and Power Supplies	Jan. p.11
VK3 V.h.f. Group Two Metre Converter	Feb. p.6
VK3 V.h.f. Group V.h.f. Pre-Amplifier	Jul. p.10
Useful Circuits using Computer Board Transistors	Sep. p.10


TECHNICAL MISCELLANEOUS

Additional Time Signal from VNG, Lyndhurst	Apr. p.7
Circuit Boards from Odds and Ends	Nov. p.18
Clock Modification for 24-Hour Movement	Nov. p.13
Conversion of Circuit Diagrams to Veroboard, Tag-Board and Printed Circuit Layout	Dec. p.12
Locally Available V.h.f. Field Effect Transistors	Feb. p.15
New Ideas on Amateur Television:	
Part One—Introduction	Apr. p.8
Part Two	May p.7
New 432 Mc. Amateur T.V. Record	Jun. p.15
New 1296 Mc. Record	Jun. p.13
Making Cabinets for Home-Built Gear	Jul. p.8
Moon Bounce	Jul. p.15
Radios of a Passing Era	Oct. p.16
"Said the Spider in the Sky"	Sep. p.8
Silver Plating of V.h.f. Inductances	Sep. p.13
Some Aspects of Radio Frequency Conductivity in Electro-Deposited Silver	Nov. p.9
The F.M. System	Dec. p.7
Transistors on Computer Circuit Boards	Aug. p.11
Some Further Thoughts	Dec. p.21
T.V.I.—It can be Eliminated . . . Well, Nearly Always	Aug. p.14
Useful Circuits using Computer Board Transistors	Sep. p.10

TRANSMITTERS

A Field-Day Transmitter	May p.8
Erratum	Aug. p.21
A Semiconductor, V.h.f. Power Amp. using a Pi-Tank Circuit	Aug. p.17
A Two Metre "Snowflake" Transistor Transmitter	Nov. p.10
A 300w. P.e.p. 2 Metre S.s.b. Transmitter	Jul. p.16
Getting Last Bit of Power from A.W.A. MR3 Carphone	May p.9
Improved F.M. Operation	Apr. p.13
Measuring Power Input and R.F. Power Output	Aug. p.15
Project—Solid State Transceiver:	
Part Three	Jan. p.8
Erratum to Part Three	Mar. p.10
Part Four	Feb. p.13
Part Five	Mar. p.8
Part Six	Apr. p.7
Part Seven	May p.10
Part Eight	Jun. p.10
Part Nine	Aug. p.8
Part Ten	Sep. p.7
Putting the Gelloso G222 on 160 Metres	Feb. p.11
Erratum (Tech. Cor.)	Apr. p.16
Sideband the Expensive Way (How to save it)	Dec. p.10
S.s.b. Transmitter—An Amateur Engineering Project:	
Part Four	Jan. p.10
Some Notes from Author	Apr. p.15
The WBNW Teeter Totter Tuners	Dec. p.17
Useful Circuits using Computer Board Transistors	Sep. p.10

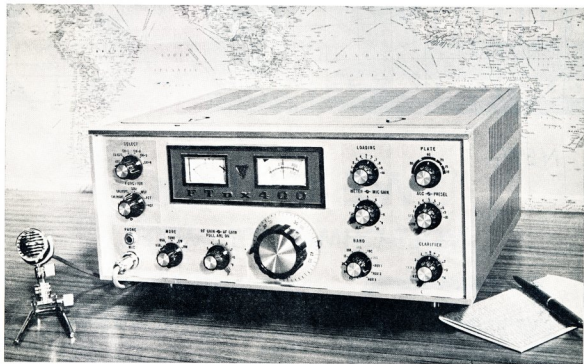Modern SSB by Yaesu! from Bail Electronic Services



TRANSCIVER MODEL FTDX-400

Latest version with all improvements, including crank handle high ratio VFO tuning control. Also has provision for power take-off and RF drive to enable use of FTV-650 six metre transverter. External VFO, FVFX-400, is available for split freq. operation.

COMPARE THE FEATURES:

- ★ Five bands, including full coverage on 10 metres.
- ★ 500-900 watts speech peak SSB input.
- ★ Power Supply built in, 230V, 50 cycles AC.
- ★ Selectable USB/LSB, CW and AM, normal or break-in keying.
- ★ Carrier input adjustable for safe tune up.
- ★ PA uses pair of new heavy duty pentodes, type 6KD6, 33 watt plate dissipation.
- ★ VOK is included, as well as PTT and panel control.
- ★ 100 Kc. and 25 Kc. dual calibrator.
- ★ Sidetone CW monitor.
- ★ Multi-scale panel meter, fully calibrated, provides direct reading of PA current, plus relative power output, ALC indication, Rx "S" units.
- ★ Offset tuning, plus or minus 5 Kc. is provided by clarifier control, which is selectable Off, Rx, Tx and Tx.
- ★ Six-pole crystal lattice filter, 2.3 Kc. bandwidth.
- ★ VFO dial readout of 1 Kc.
- ★ Dial forward reading all bands.
- ★ Provision for external VFO for split frequency operation, switch selectable for transmitting or receiving.
- ★ Receiver sensitivity better than 0.5 μ V, S/N 20 db.
- ★ Fast and slow selectable receiver AGC.
- ★ Provision for installation of optional 500 cycle CW filter.
- ★ PTT microphone included—free.
- ★ Superbly neat construction, very accessible for servicing.
- ★ Solid, charcoal blue cabinet with lift-off lid, 15 $\frac{1}{2}$ x 6 $\frac{1}{4}$ x 13 $\frac{3}{4}$ inches.
- ★ Matt finish aluminium panel.
- ★ 18 valves, 9 transistors and 33 diodes.

All sets checked before despatch. After-sales service, spares availability, 90-day warranty. All Yaesu sets sold by us are complete with plugs, power cables and English language instruction books.

FOR PRESTIGE PERFORMANCE — CHOOSE YAESU, from Bail Electronic Services

Also available, matching speaker SP-400, Ext. VFO FVFX-400, 500 cycle CW filter kit, SWR meters, co-ax. switches, 50 ohm RG-8U and RG-58AU cable, Amphenol type co-ax. connectors, Solar 24-hour digital clocks.

Pre-Christmas delivery on FTDX-400, FT-200 Transceivers, and accessories.

Sole
Australian
Agent:
BAIL ELECTRONIC SERVICES
60 Shannon St., Box Hill North, Vic., 3129. Phone 89-2213

Rep. in N.S.W.:
A. J. ("SANDY") BRUCESMITH
11 RUBY STREET, MOSMAN, N.S.W., 2088
Phone 969-8342

radioparts

PROPRIETARY LIMITED

CUSTOMER SERVICE



NEW—

"SWE-CHECK"

'VOLT-OHM-A' FET METER



- ★ **High Input Impedance:** DC volts—10 megohms per volt; AC volts—12 megohms per volt.
- ★ **Triple Overload Protection System:** Spark gap protection for accidental EHT voltages. Zener diode protection for FET circuitry. Silicon diode protection for meter movement on DC-A ranges.
- ★ **Ranges:**
DC volts—0.1, 3, 10, 30, 100, 300, 1KV and 3KV.
AC volts—0.2, 10, 30, 100, 300 and 1KV.
DC current—0.300 uA., 1 mA., 10 mA., 100 mA., and 1 A.
Ohms—R x 1 (10 ohms, centre scale) to R x 1 megohm (10 megohms, centre scale) in seven ranges.
- ★ **Accuracy:** Meter movement $\pm 2\%$ FSD. Shunts and multipliers 1%. Calibration accuracy from fully charged to discharged batteries, within 3% FSD.
- ★ **Stability:** Variation in zero setting between 16°F. to 116°F., within 3% FSD.
- ★ **Small Current Drain** (only 700 uA.).
- ★ **Polarity Change-over Switch.**
- ★ **Incorporates a 60° tilting device.** Robust construction, using fibreglass printed circuit board and plastic coated steel case. Uses long-life mercury battery.
- ★ **Dimensions:** 6 $\frac{3}{4}$ " x 8" x 3 $\frac{1}{2}$ ", exclud. handle. 3 $\frac{1}{2}$ lbs.

Price **\$99.00** + 15% S.T. where applicable



RADIO PARTS PTY. LTD.

MELBOURNE'S WHOLESALE HOUSE

562 Spencer St., Melbourne, Vic., 3000. Phone 329-7888, Orders 30-2224
City Depot: 157 Elizabeth Street, Melbourne, Vic., 3000. Phone 67-2699
Southern Depot: 1103 Dandenong Rd., East Malvern, Vic., 3145. Ph. 211-6921

OPEN SATURDAY MORNINGS!